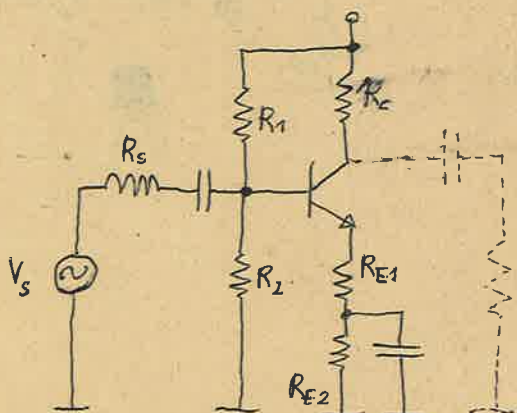


Chapter 5	186 - 214
Chapter 6	220 - 262 (566 - 571)
Chapter 7	270 - 335 (7.1, 7.3A; 7.3B excluded)
Chapter 12	519 - 547 (7.4, 7.4G ")
Chapter 8	8.4
	15.4

Vacuum Tubes (Angelo)

Brief Review

Common emitter amplifier:



DC stability:

$$S_v = \frac{dV_{ce}}{dT} = \frac{\partial V_{ce}}{\partial V_{BE}} \frac{\partial V_{BE}}{\partial T} + \frac{\partial V_{ce}}{\partial I_{CO}} \frac{\partial I_{CO}}{\partial T}$$

$$= \frac{\beta R_c}{R_B + (\beta + 1) R_E} \frac{\partial V_{BE}}{\partial T} - \frac{R_c (R_E + R_B) (\beta + 1)}{R_B + (\beta + 1) R_E} \frac{\partial I_{CO}}{\partial T}$$

For low power Si transistor neglect I_{CO} and variation w.r.t I_{CO}

$$S_i: \left. \begin{aligned} \frac{\partial V_{BE}}{\partial T} &= -2 \text{ mV}/^\circ\text{C} \\ \frac{\partial I_{CO}}{\partial T} &= 0.15 I_{CO} \end{aligned} \right\} \begin{array}{l} \text{at room} \\ \text{temp.} \\ 300^\circ\text{K} \end{array}$$

$$G_e: \left. \begin{aligned} \frac{\partial V_{BE}}{\partial T} &= -1.6 \text{ mV}/^\circ\text{C} \\ \frac{\partial I_{CO}}{\partial T} &= 0.09 I_{CO} \end{aligned} \right\} \begin{array}{l} \text{at} \\ \text{room} \\ \text{temp.} \end{array} 300^\circ\text{K}$$

Optional: $V_{CE} = \frac{V_{CC}}{2} \left(1 + \frac{R_E}{R_C + R_E} \right)$

AC considerations:

$$R_{in} = R_1 // R_2 // [r_{bb'} + (\beta + 1)(r_d + R_{E1})]$$

$$R_{out} = R_c$$

$$A_{\text{base-collector}} = \frac{-\beta(R_c // R_L)}{r_{bb'} + (\beta + 1)(r_d + R_{E1})}$$

↑ for ideal gain neglect R_L

Midband Gain:

$$A_{mid} = \frac{R_{in}}{R_{in} + R_s} A \frac{R_L}{R_c + R_{out}}$$

Bias requirements:

$$S_i \approx R_B = R_1 // R_2 \leq 0.2(\beta + 1) R_E$$

$$G_e; R_B \leq 0.1(\beta + 1) R_E$$

$$\text{If } (\beta + 1) R_{E1} \gg (\beta + 1) r_d + r_{bb'}$$

$$\text{then } A_{B-c} \approx - \frac{R_c}{R_{E1}}$$


which means A_{mid} is independent of the transistor parameters and DC conditions

Lower corner frequency:


$$\omega_{LE} = \frac{1}{C_E R_{eq}} \quad \text{where } R_{eq} =$$

$$\left\{ \frac{R_s // R_1 // R_2 + r_{bb'} + (\beta + 1) r_d + R_{E1}}{\beta + 1} \right\} // R_{E1}$$


Common base amplifier :

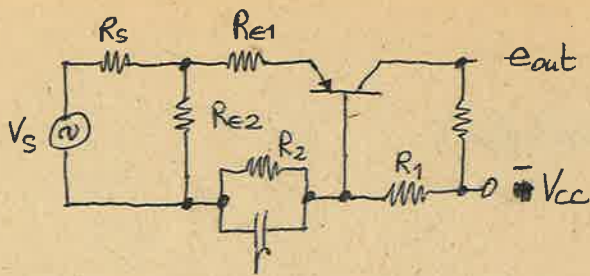

DC equivalent circuit :

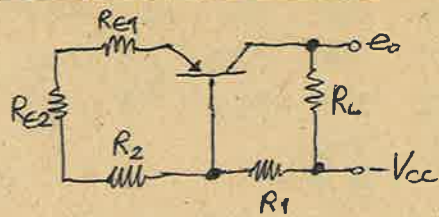

thevenin equivalent :

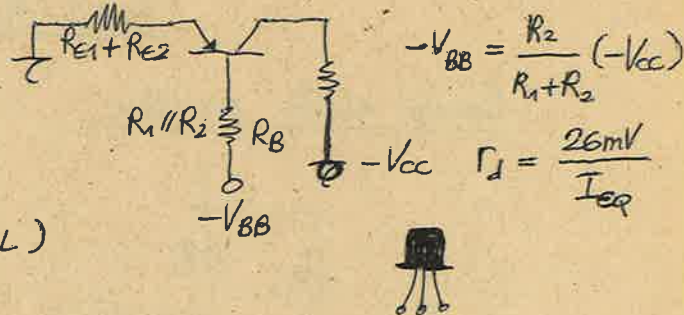


$$R_{in} = R_{e2} \parallel \left\{ R_{e1} + \left[\frac{(\beta+1)r_d + r_{bb'}}{\beta+1} \right] \right\}$$

$$= R_{e2} \parallel \left(R_{e1} + r_d + \frac{r_{bb'}}{\beta+1} \right)$$

$R_{out} = \infty$ (since current source drives R_L)

AC model :


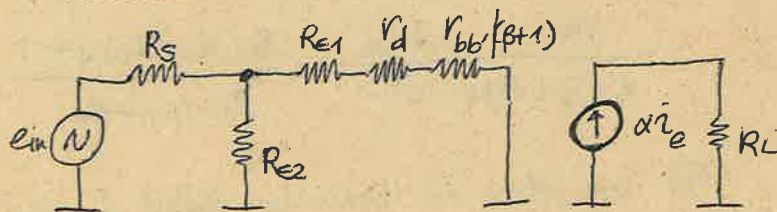


$$A_{MB} = \frac{R_s}{R_{in} + R_s} \cdot \frac{\alpha R_L}{R_{e1} + r_d + \frac{r_{bb'}}{\beta+1}}$$

(input and output are in phase)

(input impedance is comparatively low to common collector.)

Effect of low input impedance :

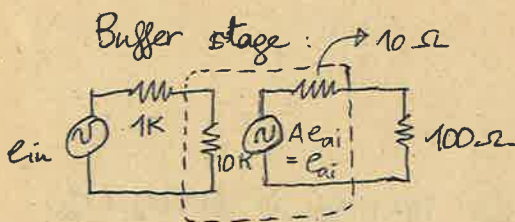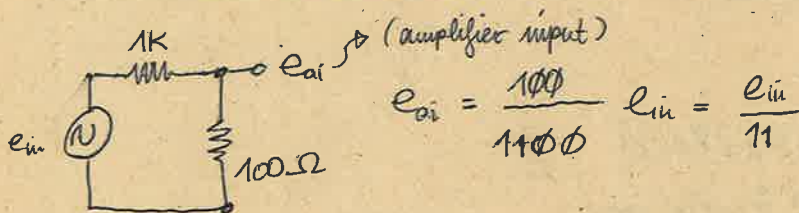


Assume gain is unity

$$e_{ai} = \frac{10}{11} e_{in}$$

$$e_{out} = \frac{100}{110} e_{ai}$$

$$e_{out} = \frac{10}{11} \cdot \frac{10}{11} e_{in} = \frac{100}{121} e_{in}$$

Common Collector (Emitter Follower)

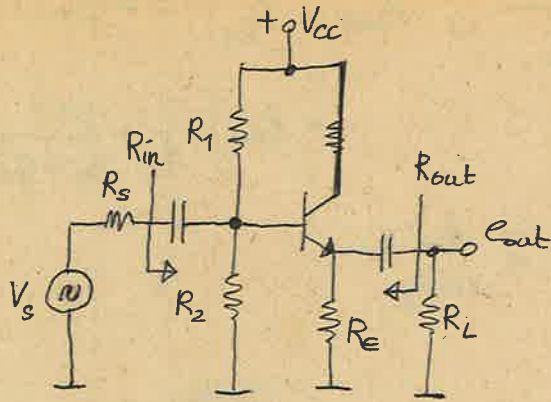

$$R_{in} = \left\{ [(R_E // R_L) + r_d](\beta + 1) + r_{bb'} \right\} // R_1 // R_2$$


$$R_{out} = \left\{ \frac{R_S // R_1 // R_2 + r_{bb'}}{\beta + 1} + r_d \right\} // R_E$$

$$R_{in} \approx [(R_E // R_L)(\beta + 1)] // R_1 // R_2 \quad (\text{usually a large resistance})$$

$$R_{out} \approx r_d // R_E \quad (\text{usually a small resistance})$$

With these properties it is usually used as a buffer stage.

Small signal model:

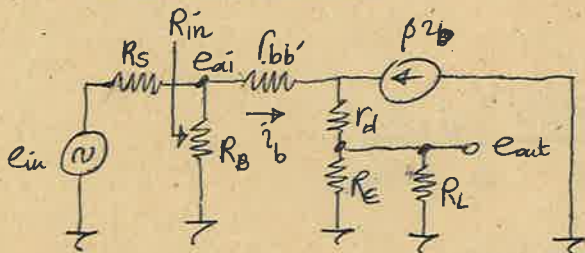

Midband gain: $A_{MB} = \frac{R_{in}}{R_{in} + R_S} \cdot A_{B-E}$

$$A_{B-E} = \frac{(\beta + 1)(R_E // R_L)}{[r_{bb'} + r_d + (R_E // R_L)](\beta + 1)} \approx 1$$

$$\Rightarrow A_{MB} \approx \frac{R_{in}}{R_{in} + R_S}$$


If $R_{in} \gg R_S : A_{MB} \approx 1$

(Voltage gain is always less than unity)


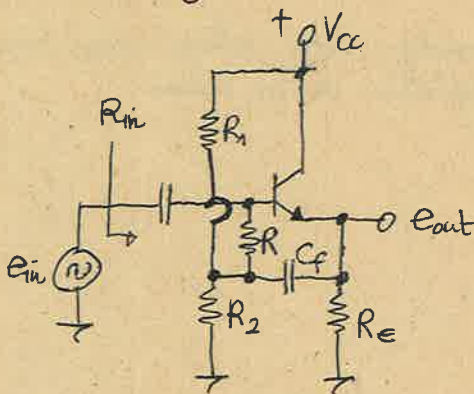
Problem of emitter follower:

If R_B is low (R_1 and R_2) this may cause overall R_{in} to be low.


The following circuit called "bootstrap circuit" overcomes this discrepancy:



DC equivalent circuit:

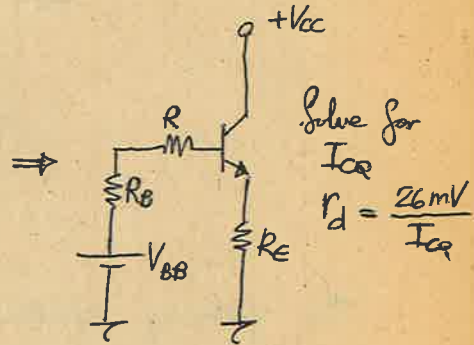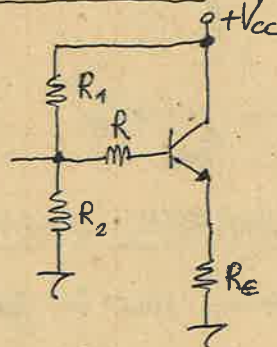

Small signal equivalent circuit:

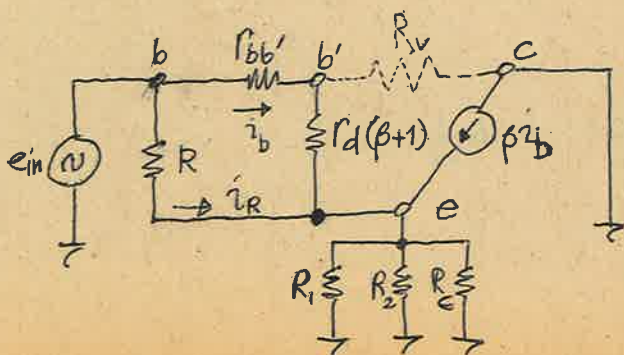

r_v is the internal resistance between b' and c . It is in the order of $M\Omega$'s
 Let $R_{eq} = R_1 // R_2 // R_E$

$$i_R = \frac{e_{in} - e_{out}}{R}, \quad i_b = \frac{e_{in} - e_{out}}{r_{bb'} + (\beta+1)r_d}, \quad e_{out} = R_{eq} [i_r + (\beta+1)i_b]$$

$$= R_{eq} \left[\frac{1}{R} + \frac{\beta+1}{r_{bb'} + (\beta+1)r_d} \right] (e_{in} - e_{out})$$

$$\frac{e_{out}}{e_{in}} = \frac{R_{eq} \left[\frac{1}{R} + \frac{(\beta+1)}{r_{bb'} + (\beta+1)r_d} \right]}{1 + R_{eq} \left[\frac{1}{R} + \frac{(\beta+1)}{r_{bb'} + (\beta+1)r_d} \right]} \approx 1 \text{ less than unity.}$$

STAFFBO

$$e_o = A_{MB} e_{in}$$

$$i_{in} = i_b + i_R$$

$$i_b = \frac{e_{in} - e_{out}}{r_{bb'} + (\beta+1)r_d} = \frac{1 - A_{MB}}{r_{bb'} + (\beta+1)r_d} e_{in}$$

$$i_R = \frac{e_{in} - e_{out}}{R} = \frac{1 - A_{MB}}{R} e_{in}$$


$$i_{in} = i_b + i_R \Rightarrow R_{in} = \frac{e_{in}}{i_{in}} = \left[\frac{r_{bb'} + (\beta+1)r_d}{1 - A_{MB}} \right] \parallel \frac{R}{1 - A_{MB}}$$

$$= \frac{[r_{bb'} + (\beta+1)r_d] \parallel R}{1 - A_{MB}}$$

Since $A_{MB} \approx 1$, R_{in} is quite high. If R_{in} is in the order of $M\Omega$'s, actual input impedance (neglecting $r_{bb'}$)

$$R_{in} = \left[\frac{(\beta+1)r_d \parallel R}{1 - A_{MB}} \right] \parallel r_v$$

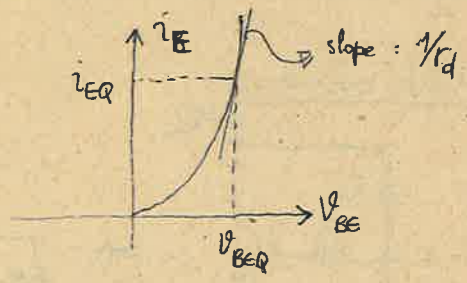- Another problem of the emitter follower stage is to amplify large voltage swings. It is due to the nonlinear behavior of the base emitter junction.




To amplify large voltage swings, some other configurations can be utilized.

AMPLIFIER DESIGN :

The following specifications must be given :

- The midband voltage gain, A_{MB}
- The stability factor.
- Power supply voltage.
- Frequency band over which the amplifier is to be used.
- Max. output voltage swing
- Load impedance. (a.c or d-c coupled)
- Source impedance.

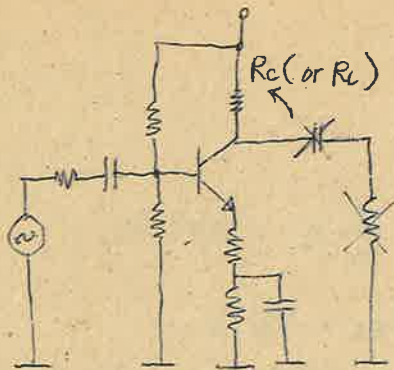Assumed you decided on a common emitter stage:



If the load is not specified as a.c or d.c coupled, Choose R_C or R_L .

Supply voltage V_{CC} is also given. Choose a Q-point.

- Your Q-point determines I_{CQ} ;

- Then calculate r_d ;

- Set $R_B = 0.2(\beta+1)R_E$ (SI);

$$R_{in} = R_B \parallel [r_{bb'} + (\beta+1)(r_d + R_{E1})]$$

$$\approx R_B \parallel (\beta+1)R_{E1}$$

- Now assume $R_{E2} = 0$, then $R_{E1} = R_E$

$$\text{So } R_{in} \approx R_B \parallel (\beta+1)R_E$$

$$= \frac{R_B(\beta+1)R_E}{R_B + (\beta+1)R_E} = \frac{[0.2(\beta+1)R_E](\beta+1)R_E}{[0.2(\beta+1)R_E + (\beta+1)R_E]}$$

$$= \frac{(0.2)(\beta+1)R_E}{1.2}$$

$$- A_{MB} = \frac{R_{in}}{R_{in} + R_S} = \frac{R_L}{R_L + R_C} \cdot A \quad \rightarrow \text{ideal voltage gain}$$

$$A = \frac{-\beta R_C}{r_{bb'} + (\beta+1)(r_d + R_{E1})}$$

$$\approx \frac{-\beta R_C}{(\beta+1)R_E}$$

So A and R_{in} are functions of R_E only.

$$A_{MB} = A_{MB}(R_E)$$

Given A_{MB} , solve for R_E

Then determine R_B and considering I_{BQ} , determine R_1, R_2 .

R_{E1}, R_1, R_2 are now determined;

If you are given S_v , check whether your R_E satisfies this S_v or not. If not you can conclude that $R_{E2} \neq 0$.

$$\text{First calculate } S_v = \frac{\beta R_C}{R_B + (\beta+1)R_E} \frac{dV_{BE}}{dT} = \frac{\beta R_C}{1.2(\beta+1)R_E} \frac{dV_{BE}}{dT}$$

calculate R_E


Then consider A_{MB} then calculate R_{E1}

If means some of the emitter resistance is not bypassed. Determine R_E from S_v .

$R_{E2} = R_E - R_{E1}$

Study examples : 5.3, 5.4, 5.5, 5.6

DC AMPLIFIERS:


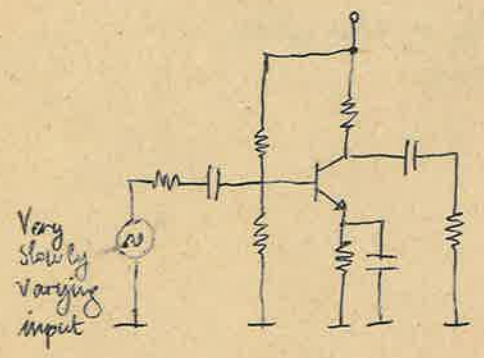


$f_{o, input} = \frac{1}{100} \text{ Hz} = 0.01 \text{ Hz}$




Assume ; $f_{E2} = 100 \text{ Hz}$.

This amplifier will hardly amplify this input. To amplify that signal capacitors should be replaced by circuits \swarrow short.

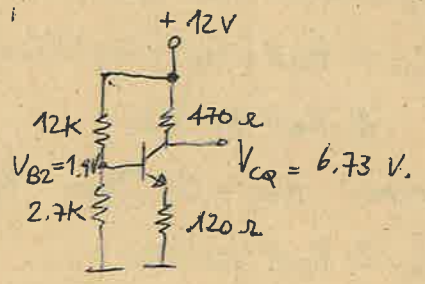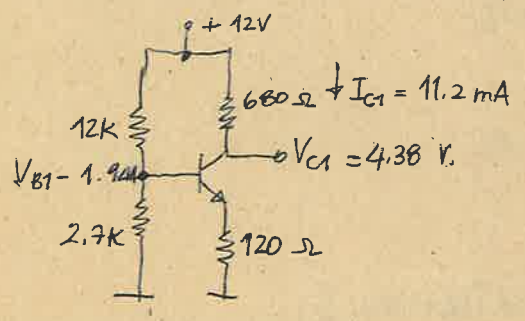Consider the following common emitter stages :



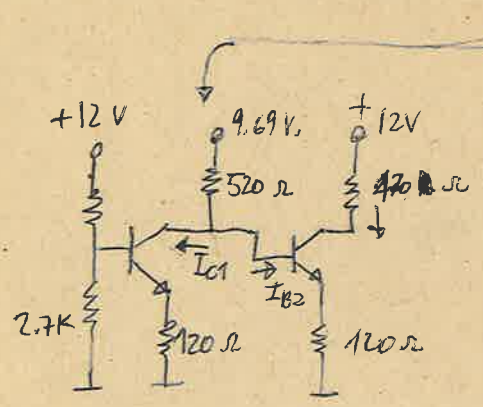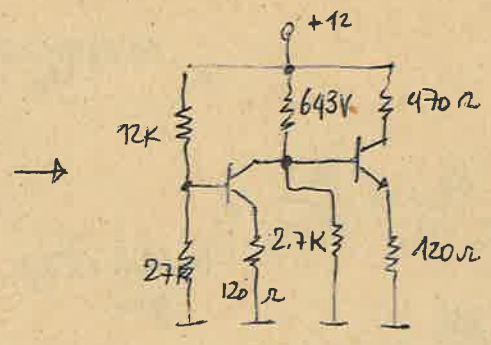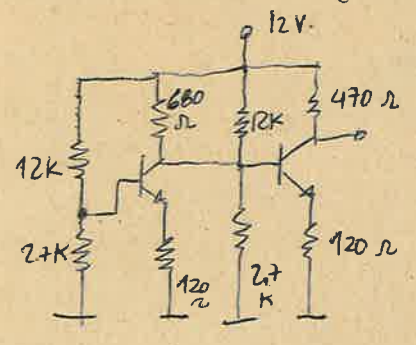Assumed collector 1 of the first stage is connected to the base of the second.




$I_{C1} = 11.2 \text{ mA}$
 $V_{C1} = 9.69 - (520 \Omega \times 11.2 \text{ mA})$
 $= 3.866 \text{ V (neglecting } I_{B2})$

The circuits in which a d.c signal is amplified along a.c signal are called d.c amplifiers. Capacitors cannot be used between the stages of a d.c amplifier. Two major problems arise in designing amplifiers without coupling capacitors.


- The biasing of each stage is dependent on adjacent stages.
- Temperature stability is often poor. Since the drift component of the first stages are amplified by succeeding stages.

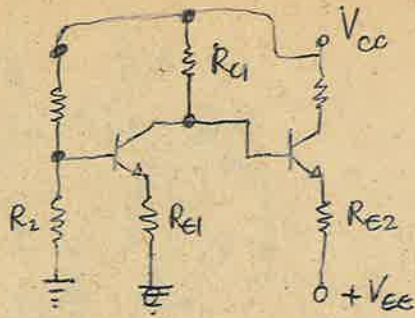To keep the base and collector voltages at the desired levels the following configuration can be used:



Assume I_{B2} is negligible $V_{BE2} + I_E R_{E2} = V_{C1} - V_{EE}$

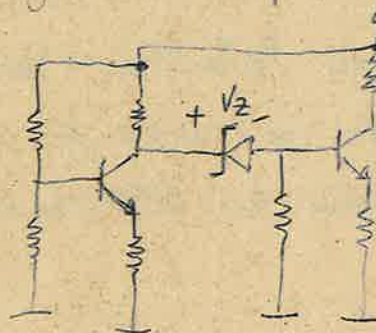
The disadvantage of this circuit is to use another supply voltage. The following circuit can be proposed:



$$V_{B2} = V_{C1} - V_2$$

DIFFERENTIAL AMPLIFIERS

24 APR 80

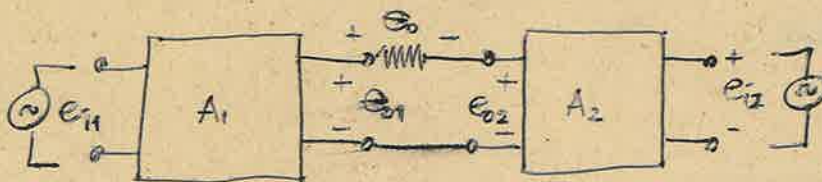

$$e_o = e_{o1} - e_{o2}$$

$$= A_1 e_{i1} - A_2 e_{i2}$$

Common mode: $e_{i2} = e_{i1} = e_i$

Common mode gain: $e_o = \underbrace{(A_1 - A_2)}_{\text{Common mode gain}} e_i$

$$\text{If } A_1 = A_2 \Rightarrow e_o = 0$$



Differential amplifiers have good temperature stability since the output is measured as the difference of two outputs.

Differential mode gain:

In general $e_{i1} \neq e_{i2}$;

$$A_{DM} = \frac{e_{out}}{e_{i1} - e_{i2}}$$

A differential amplifier with BJT's:

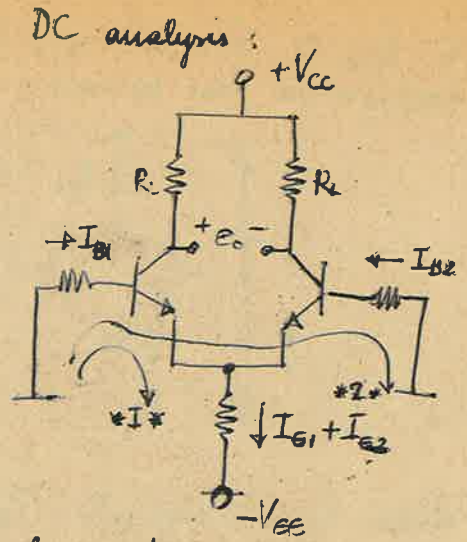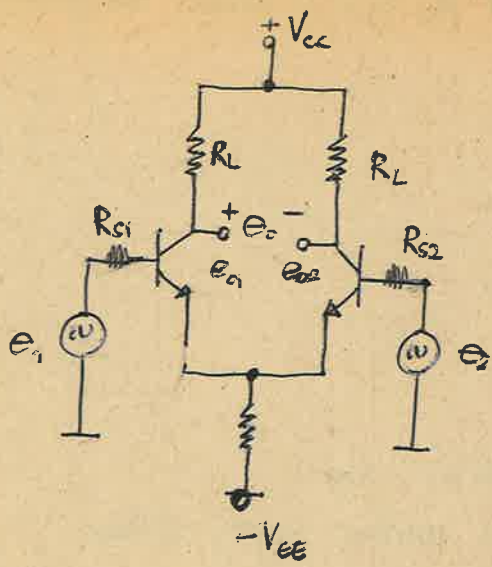

loop equations:

1 $R_s I_{B1} + V_{BE1} + R_E [(\beta+1)I_{B1} + (\beta+1)I_{B2}] - V_{EE} = 0$

2 $R_s I_{B1} + V_{BE1} = V_{BE2} + R_s I_{B2}$

Solve for 1 and 2 for I_{B1} and I_{B2}

Assume two BJT's are equal: $\beta_1 = \beta_2 = \beta$

$V_{BE1} = V_{BE2} = V_{BE}$


Also assume $R_{s1} = R_{s2} = R_s$

$R_s I_B + V_{BE} + 2I_E R_E - V_{EE} = 0$

$I_B = \frac{V_{EE} - V_{BE}}{R_s + 2(\beta+1)R_E}$

$V_{CQ1} = V_{CQ2} = V_{CC} - \beta I_B R_L$ The d.c value of the output voltage will be zero if two stages are identical.

Small signal model:

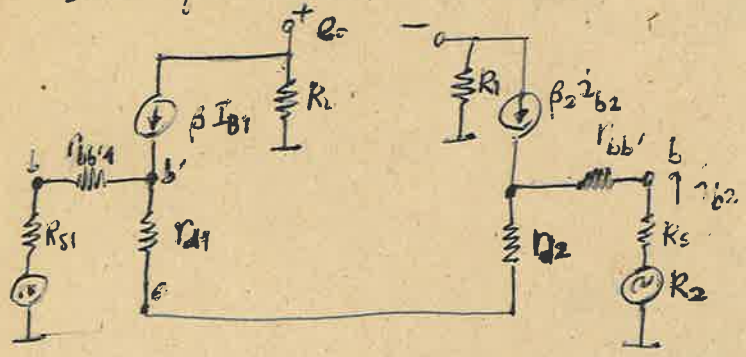

Usually $R_E \gg r_{d1} + \frac{R_{s1} + r_{bb1}}{\beta_1 + 1}$, $r_{d2} + \frac{r_{bb2} + R_{s2}}{\beta_2 + 1}$

Therefore it can be assumed as open ckt.

Apply superposition:

Set $e_2 = 0$

$i_{b1} = \frac{e_1}{R_{s1} + r_{bb1} + (\beta_1 + 1) [r_{d1} + r_{d2} + \frac{r_{bb2} + R_{s2}}{\beta_2 + 1}]}$

$i_{e1} = -i_{e2}$

Assume identical stages:

$$i_{b1} = \frac{e_1}{R_s + r_{bb'} + (\beta+1) \left[2r_d + \frac{r_{bb'} + R_s}{\beta+1} \right]}$$

$$i_{b1} = \frac{e_1}{2[R_s + r_{bb'} + (\beta+1)r_d]}$$

Since $\beta_1 = \beta_2 = \beta$

$$i_{e1} = -i_{e2} \Rightarrow i_{b1} = -i_{b2}$$

$$i_{b2} = \frac{-e_1}{2[R_s + r_{bb'} + (\beta+1)r_d]}$$

$$e_o = -R_L \beta i_{b1} - (-R_L \beta i_{b2})$$

$$e_{o1} = -R_L \beta i_{b1}$$

$$e_{o2} = -R_L \beta i_{b2}$$

$$\frac{e_{o1}}{e_1} = \frac{-R_L \beta}{2[R_s + r_{bb'} + (\beta+1)r_d]} \Big|_{e_2=0}$$

$$\frac{e_{o2}}{e_2} = \frac{(-R_L \beta)(-1)}{2[R_s + r_{bb'} + (\beta+1)r_d]} = \frac{R_L \beta}{2[R_s + r_{bb'} + (\beta+1)r_d]} \Big|_{e_2=0}$$

With $e_2 = 0$ e_{o1} is inverting output e_{o2} is non inverting output.

$$\frac{e_{o1} - e_{o2}}{e_1} = \frac{R_L \beta}{R_s + r_{bb'} + (\beta+1)r_d}$$

Similarly

$$\frac{e_{o1}}{e_2} \Big|_{e_1=0} = \frac{R_L \beta}{2[R_s + r_{bb'} + (\beta+1)r_d]}$$

$$\frac{e_{o2}}{e_1} \Big|_{e_2=0} = \frac{-R_L \beta}{2[R_s + r_{bb'} + (\beta+1)r_d]}$$

So if $e_1 \neq 0$, $e_2 \neq 0$

$$e_{o1} = \frac{-R_L \beta}{2[R_s + r_{bb'} + (\beta+1)r_d]} (e_1 - e_2)$$

$$e_{o2} = \frac{R_L \beta}{2[R_S + r_{be'} + (\beta + 1)r_d]} (e_1 - e_2)$$

$$e_o = e_{o1} - e_{o2}$$


$$= \frac{-R_L \beta}{R_S + r_{be'} + (\beta + 1)r_d} (e_1 - e_2)$$

ADM
Differential mode
gain

Common mode gain:

$$e_o = 0$$

DC stability:

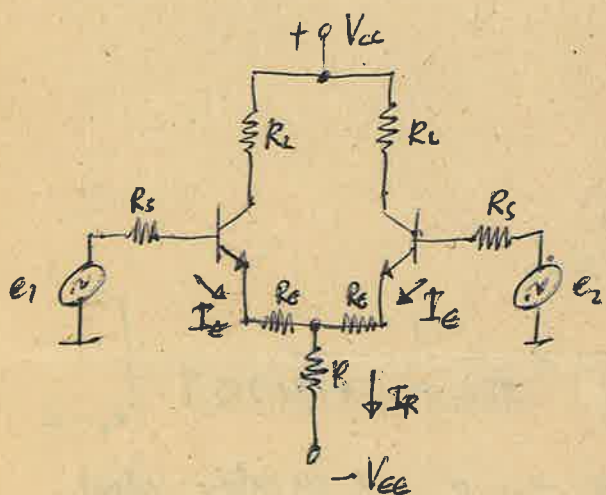


$$I_E = \frac{I_R}{2}$$

$$\Rightarrow \Delta I_E = \frac{\Delta I_R}{2}$$

If ΔI_R is kept at 0 ;
(i.e constant I_R) then perfect
stability reached.

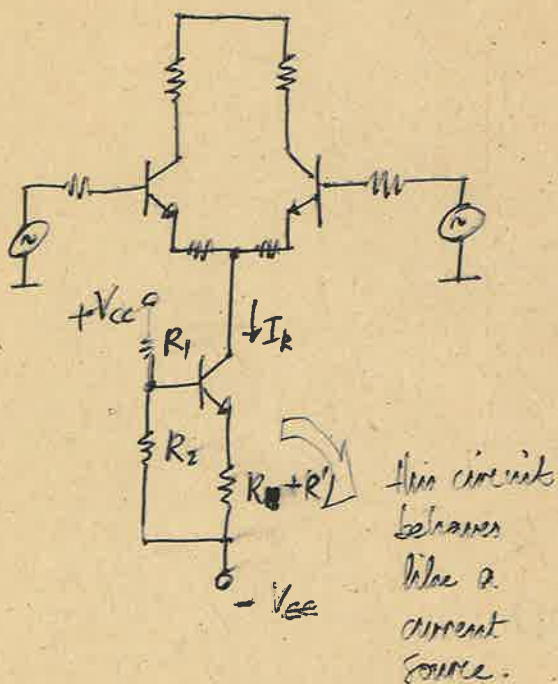Assume R is removed and a current source is connected there.




The resistor R is a temperature
dependent resistor with a positive
temperature coeff.

$$\frac{dR/dT}{R} = \gamma \text{ (temperature coefficient)}$$

$$\frac{dR}{dT} = \gamma R \text{ (}\gamma > 0\text{)}$$

R' is a constant resistor.

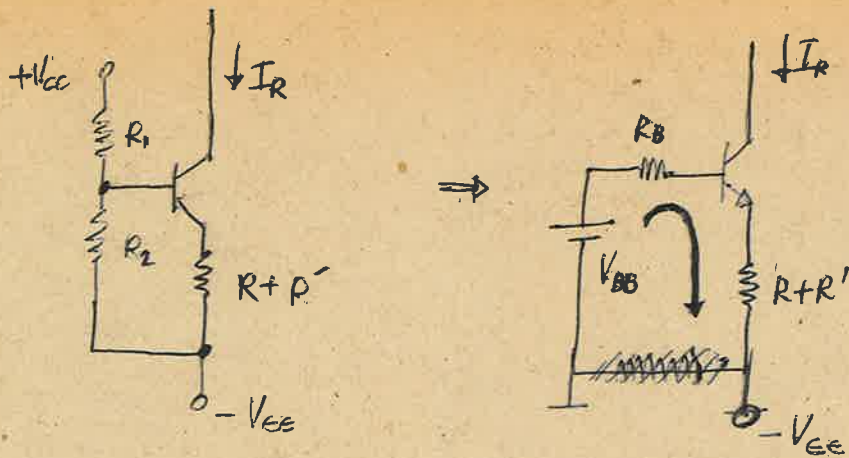

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{cc} + \left(-\frac{R_1}{R_1 + R_2} V_{ee} \right)$$

$$R_B = R_1 || R_2$$

Assume a silicon transistor

$$\frac{dI_R}{dT} = \frac{\partial I_R}{\partial V_{BE}} \frac{\partial V_{BE}}{\partial T}$$

$$I_B = \frac{V_{BB} + V_{ee} - V_{BE}}{R_B + (\beta + 1)(R + R')}$$

$$I_R = \beta I_B = \frac{\beta(V_{BB} + V_{ee} - V_{BE})}{R_B + (\beta + 1)(R + R')}$$

$$\frac{dI_R}{dT} = \frac{-\beta}{R_B + (\beta + 1)(R + R')} (-0.002) + \frac{\beta(V_{BB} + V_{ee} - V_{BE}) [-(\beta + 1)]}{[R_B + (\beta + 1)(R + R')]^2} \frac{dR}{dT}$$

$\frac{dR}{dT} = \gamma R$

$$\frac{dI_R}{dT} = 0 \Rightarrow \beta(0.002)[R_B + (\beta + 1)(R + R')] - \beta(\beta + 1)(V_{BB} + V_{ee} - V_{BE})\gamma R = 0$$

$$R = \frac{(0.002)[R_B + (\beta + 1)R']}{(\beta + 1)[\gamma(V_{BB} + V_{ee} - V_{BE})] - 0.002}$$

5.27 For reasonable stability $A \approx 10$

$$A_o = A_1 \times A_2 \times \dots \times A_n$$

Assumption: $A_1 \approx A_2 \approx A_3 \Rightarrow A_o = A^n$

$$A^n = 1000 \Rightarrow 3 \text{ found.}$$

5.28 $n = 3-4$

5.29 $A_o = A^n$


for $A = 10$ $n = 2$ leads to $A_o = 100$

$n = 3$ " " $A_o = 1000$

Since $A = 400$ is the wanted gain we choose $n = 3$

5.30 $n = 5-6$

5.31

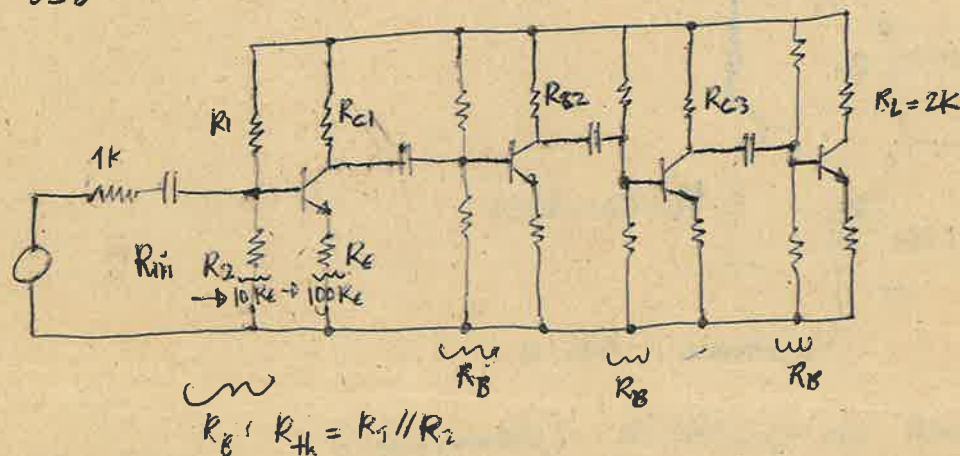

Assumption: $\beta + 1 = 100$

Assumption: $R_2 = 10R_e$

$$R_{in} \approx 10R_e \parallel 100R_e = 9.09R_e$$

$$A_o = \frac{9.09R_e}{R_1 + 9.09R_e} A_{bc1} \frac{9.09R_e}{R_{c1} + 9.09R_e} A_{bc2} \frac{9.09R_e}{R_{c2} + 9.09R_e} A_{bc3} \frac{9.09R_e}{R_{c3} + 9.09R_e} A_{bc4}$$

first Attenuation
second Attenuation
third
fourth

$$A_o = \frac{(9.09R_e)^4 \left(\frac{R_c}{R_e}\right)^3 \left(\frac{R_c}{R_e}\right)}{(R_1 + 9.09R_e)(R_c + 9.09R_e)^3} = 1000 \quad (.1000 \text{ is given})$$

Assume $R_e = 300$

So $R_c = 5.037 \text{ k}$ or assume $R_c = 400 \Omega$ then $R_e = 8.383 \text{ k}$.

5.32 $R_E = 300 \Omega$
 $R_C = 2.2 \text{ k}\Omega$


5.34 $A_{MB} = 104$

Set $n = 5$

Assume $R_E = 300$


$R_C = 7.79 \text{ k}\Omega$

5.35 :

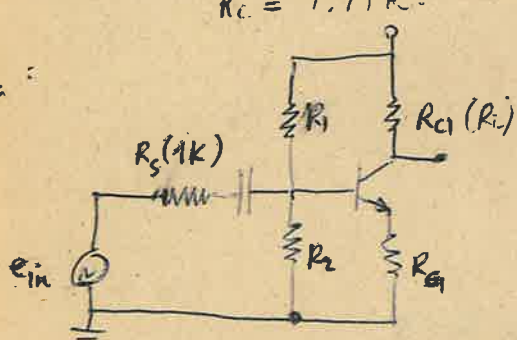

$$A_{max} = \frac{\beta R_L}{R_s + r_{be} + (\beta + 1)(R_E + R_C)} = -\beta$$

neglect

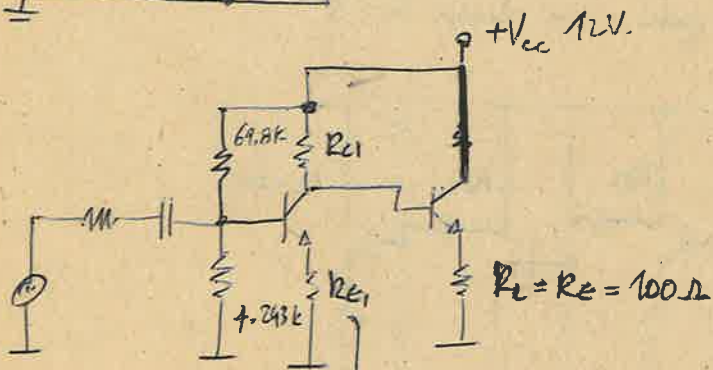


Assume: 150Ω

$I_B = 0.5 \text{ mA} \Rightarrow r_d = 52 \Omega$ (Assumption)

then $R_C = 14.91 \text{ k}\Omega$
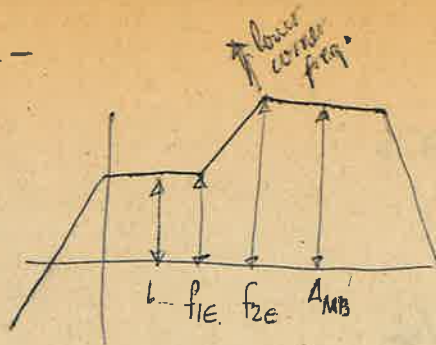
$$A_{MB} = A_{dc} \frac{f_{\beta 2E}}{f_{\beta 1E}}$$



$$f_1^0 = \frac{f}{\sqrt{2^{1/n} - 1}}$$


corner frequency.

$$S_v = \frac{\frac{1.062 \text{ V/C}}{dT} \beta R_c}{R_B + (1 + \beta) R_E}$$

base transfer resistance βR_c unbypassed

$$A_v = \frac{\beta R_c}{r_{be} + R_B + (\beta + 1)(r_d + R_E)} \approx \frac{R_c}{R_E}$$


AC Load.

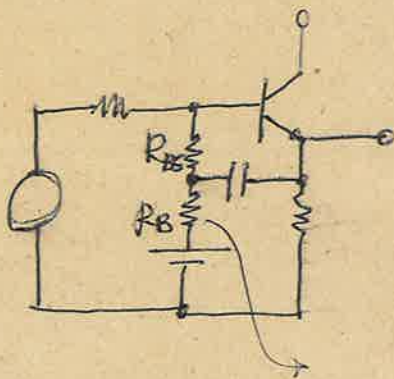

$$R_{BS} = \frac{R}{1 - A_v}$$

$$A_c = \frac{1 + \beta}{1 + \frac{R_{in}}{R_B}}$$

↳ nearly unity in common collector amp.

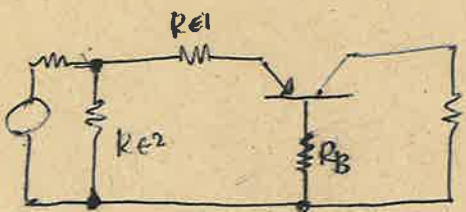


$$A_c \text{ current gain} = \frac{\alpha}{1 + \frac{R_{in}}{R_{E2}}}$$

5.40 $C_{C1} = 1 \mu F$
 $C_{C2} = 1 \mu F$

$$f_1 = \frac{1}{2\pi C_{C1} (R_S + R_{in1})} = 17.78 \text{ Hz}$$

$$f_1' = \frac{1}{2\pi C_{C2} (R_{C1} + R_{in2})} = 11.04 \text{ Hz}$$

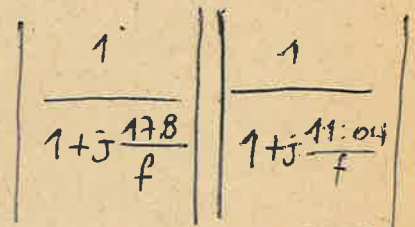jumlah corner corner $\frac{1}{\sqrt{2}}$ atau $\sqrt{2}$



$f = 22.632 \text{ Hz}$
 data terbesar di-ali.

AR one plus or single proportional slope n

5.41

$$f_{2e} = 4107.7$$

5.425.43

Sindirik geselin

5.445.45

güç mark

5.46

↑

5.475.50

Örneği

$$V_{out} = I_{e2} R_2$$

$$\frac{R_2}{R_1} (V_{CC} - V_{in} - V_{BE})$$

3.4V.

$$\frac{R_2}{R_1} = 0.588$$

5.51

Çözüm

57 Ω.

5.52

106 Ω.

5.53

19 Ω

5.54

Ex 5.7 ye göre

$$R + R_1 = 1490 \Omega$$

$$R_1 = 28.35 R$$

$$R = 50.7 \Omega$$


$$R_1 = 1439.3 \Omega$$

} örneği


NOISE

The noise in the amplifiers are due to a) semiconductors
b) resistors

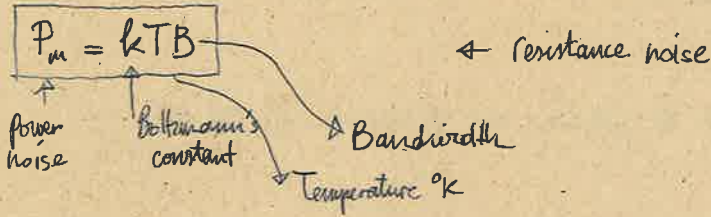Noise equation developed by Nyquist in 1928 :



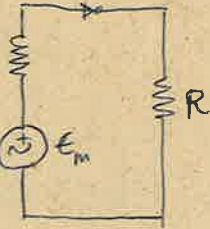
This noisy resistor can be considered noise-free now and delivering noise power P_m to another resistor R




$$P_m = \frac{E_m^2}{4R} = kTB$$

$$E_m = \sqrt{4kTB R}$$

1/f noise

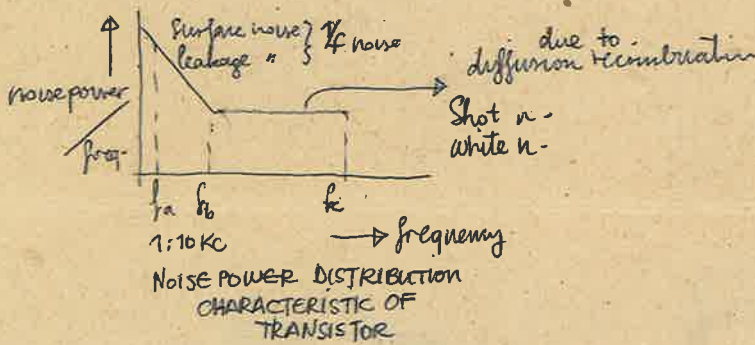

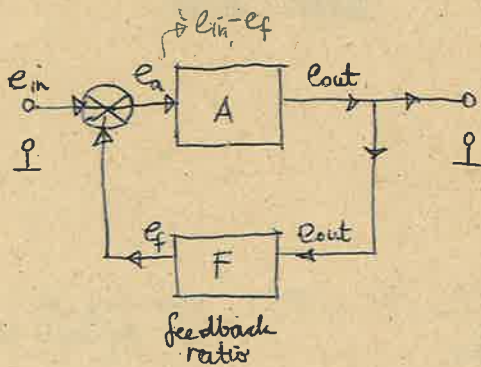The noise can be suppressed by a feedback network :



$$e_{out} = A e_a$$

$$= A(e_{in} - e_f)$$

$G \triangleq \frac{e_{out}}{e_{in}}$ *am uaktaki voltajin en yakindaki voltajga oran*

$F \triangleq \frac{e_f}{e_{out}}$ *"her gain uktasin qoise oran o larak atqulir"*

$$G = \frac{A(e_{in} - e_f)}{e_{in}}$$

$$G = \frac{A}{1 + AF} \approx \frac{1}{F} \text{ when } AF \gg 1$$

So G is almost independent of A

SENSITIVITY :

if x is a function of y :

$$S_{x,y} = \frac{dx/x}{dy/y} = \frac{y}{x} \frac{dx}{dy}$$

Answer of Prob 6 : n1.17

$$G = G(A(T), F(T))$$

gain is function of A and F which are function of T .

$$S_{G,A} = \frac{A}{G} \frac{dG}{dA}$$

$$S_{G,F} = \frac{F}{G} \frac{dG}{dF}$$

$$S_{G,T} = \frac{T}{G} \frac{dG}{dT}$$

$$S_{A,T} = \frac{T}{A} \frac{dA}{dT}$$

$$S_{F,T} = \frac{T}{F} \frac{dF}{dT}$$

$$\frac{dG}{dT} = \frac{dG}{dA} \frac{dA}{dT} + \frac{dG}{dF} \frac{dF}{dT}$$

After some substitution :

$$S_{G,T} = S_{G,A} S_{A,T} + S_{G,F} S_{F,T}$$

Temperature coefficient of gain :

$$(TC)_G = \frac{dG/G}{dT}$$

$$(TC)_G = S_{G,A} (TC)_A + S_{G,F} (TC)_F$$

Signal to noise ratio (SNR)

$$(SNR) = \frac{e_s}{e_m}$$

$$(SNR)_a = \frac{A e_s}{e_{am}} \quad \text{open loop amplifier}$$

$$(SNR)_f = \frac{A e_s}{e_{gm}} = \frac{A e_s}{e_{am}/(1+AF)} = \frac{A e_s}{e_{am}} (1+AF)$$

improving the signal to noise ratio by using feedback.


$$\left\{ e_{gm} = \frac{e_{am}}{1+AF} \right\}$$

Second improvement about bandwidth :

$$A = \frac{A_{MB}}{1 + j\omega/\omega_2}$$

putting $G = \frac{A}{1+AF}$:
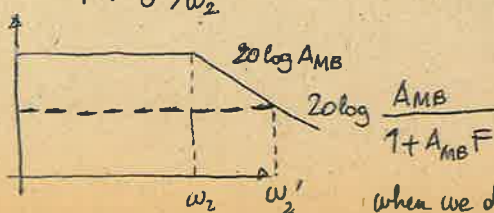
$$G = \frac{A_{MB}}{1 + A_{MB}F} \cdot \frac{1}{1 + j\frac{\omega}{\omega_2(1+AF)_{MB}}}$$



$$\omega_2' = \omega_2 (1 + A_{MB}F)$$


$$A_{MB} \omega_2 = GBW$$

when we decrease the gain, increase the bandwidth

Feedback also modifies the input and output impedances of circuit-

Types of feedback:

$F_{v,v}$	v/v	voltage transfer ratio
$F_{v,i}$	v/i	impedance
$F_{i,v}$	i/v	admittance
$F_{i,i}$	i/i	current transfer ratio

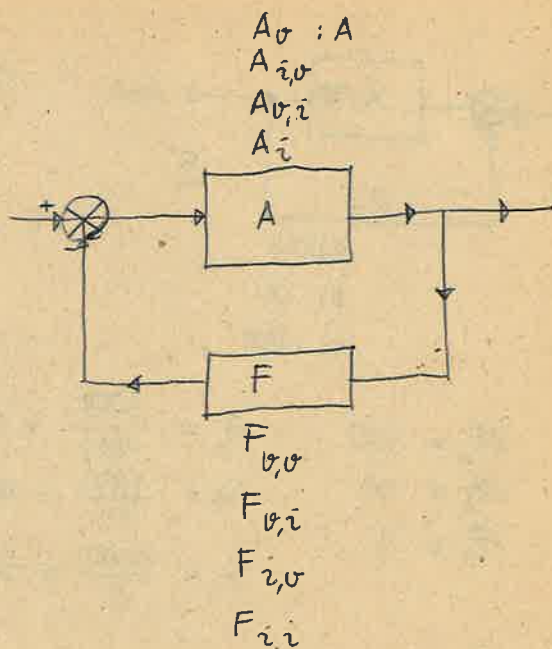

$$\frac{e_{out}}{e_{in}} = G = \frac{A}{1 + AF_{v,v}}$$


$$\frac{i_{out}}{e_{in}} = G_{i,v} = \frac{A_{i,v}}{1 + A_{i,v}F_{v,i}}$$

transadmittance of the circuit


$$\frac{e_{out}}{i_{in}} = G_{v,i} = \frac{A_{v,i}}{1 + A_{v,i}F_{i,v}}$$

transimpedance of the circuit

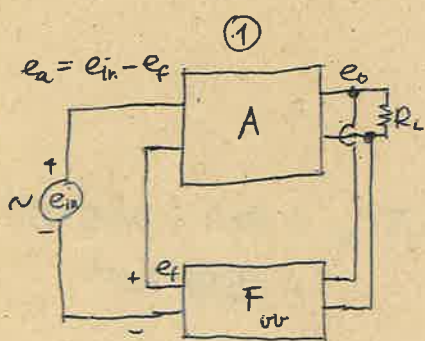
$$\frac{i_{out}}{i_{in}} = G_i = \frac{A_i}{1 + A_i F_{i,i}}$$




voltage series feedback

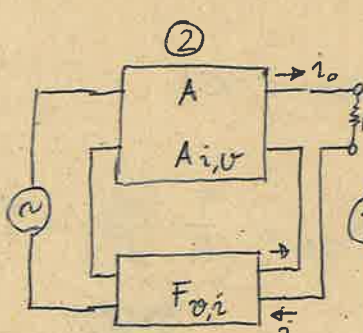

current series feedback
transadmittance

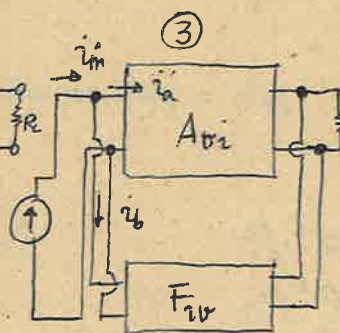

transimpedance
voltage shunt amp.

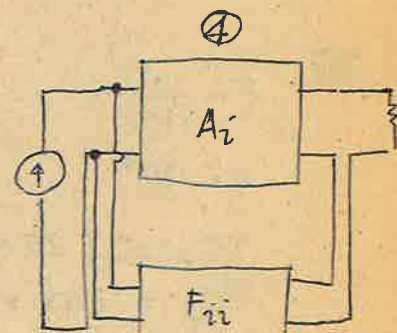

current shunt amplifier
current ratio amplifier

series shunt ① ② : $R_{in} = R_{ia}(1 + AF_w)$ input impedance increased.


series shunt ③ ④ : $R_{in} = \frac{R_{ia}}{(1 + A_{v,i}F_{i,v})}$ input impedance decreased

voltage shunt ① ③ : $R_o = \frac{R_{oa}}{1 + F_{v,v}A}$ output impedance decreased

current shunt ② ④ : $R_o = R_{oa}(1 + A_{i,v}F_{v,i})$ output impedance increased

PROBLEMS (CHAPTER 6)

①

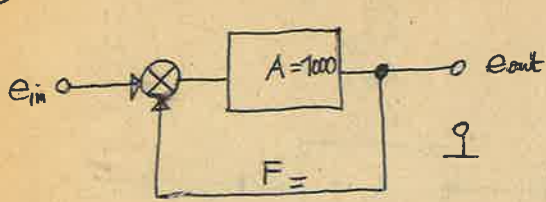

$$G = \frac{A}{1+AF}$$

$$AF \gg 1 \Rightarrow G \cong \frac{1}{F}$$

- a) 0.1
- b) .01
- c) .001

$AF_a = 100$	$G_a = \frac{1000}{101} = 9.9 \approx \frac{1}{F_a} = 10$
$AF_b = 10$	$G_b = \frac{1000}{11} = 90.9 \approx \frac{1}{F_b} = 100$
$AF_c = 1$	$G_c = \frac{1000}{2} = 500 \neq \frac{1}{F_c} = 1000$

②

$$G = \frac{1000}{1+1000F} = 50 \Rightarrow F = 0.019$$

③

$$x = 101y + 10y^2$$

find S at y=2

$$S_{x,y} = \frac{y}{x} \frac{dx}{dy}$$

$y_0 = 2$
 $x_0 = 242$

$$\frac{dx}{dy} = 20y + 101$$

$$S_{x,y} = 1.1653$$

④

$$F = \frac{1}{100} \quad \text{ppm} = \text{parts per million} = 10^{-6}$$

$$A = 10^4$$

$$TC_F = \pm 25 \times 10^{-6} / ^\circ\text{C}$$

$$TC_A = 3000 \times 10^{-6} / ^\circ\text{C}$$

$$TC_G = 54.5 \times 10^{-6} / ^\circ\text{C}$$

$$S_{G,T} = \left(\frac{T}{G} \right) \left(\frac{dG}{dT} \right) = T \times TC_G = 300\text{K} \times 54.5 \times 10^{-6} = 16350 \times 10^{-6}$$


temperature
sensitivity
coefficient

⑤

$$6.3 \quad S_{G,A} = \frac{1}{1+AF}$$

$$S_{G,F} = \frac{AF}{1+AF}$$

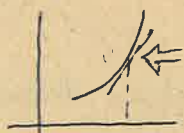Answer: All sensitivity values are not valid for large changes.




⑥

$$e = \underbrace{10 \cos 2000\pi t}_{\text{1st Harmonic}} + \underbrace{0.2 \cos 4000\pi t}_{\text{2nd}} + \underbrace{0.1 \cos 6000\pi t}_{\text{3rd}}$$

distortion factor:
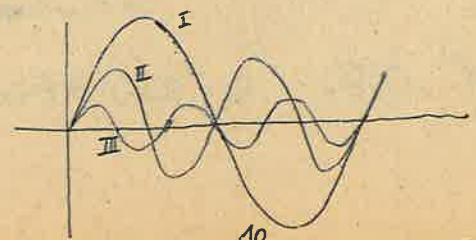
$$D = \frac{E_1 \text{ fundamental}}{\sqrt{\sum_{k=2}^m E_k^2}} = \frac{E_1}{\sqrt{E_2^2 + E_3^2 + \dots + E_m^2}}$$



$$SNR = D = \frac{10}{\sqrt{0.2^2 + 0.1^2}} = 44.72$$

7

$$e_{in} = 0.1 \sin 2000\pi t$$

$$A = 200$$

open loop $\rightarrow e_{out} = 20 \sin 2000\pi t + 0.3 \cos 4000\pi t$
 e_s e_{in} \uparrow Second harmonic coming out "distortion"

$$(SNR_1) = \frac{20}{0.3} = 66.7$$

Signal to noise ratio of the open loop amplifier

$$G = \frac{A}{1+AF} = \frac{200}{1+200 \times 0.1} = 9.524$$


closed loop $\rightarrow e_{out} = 20 \sin 2000\pi t + B \cos 4000\pi t$

$$B = \frac{0.3}{21} = 0.0143$$

$$(SNR_2) = \frac{20}{0.3/21} = 1400$$

Signal to noise ratio of closed loop amplifier.

8

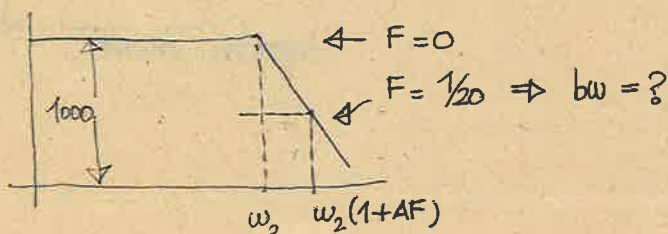


$$\omega_{2F} = 51 \times 10^7 \text{ rad/sec}$$

9

$$F = \frac{\frac{1/20}{0.05}}{1 + j \frac{\omega}{10^7}}$$

$$G = \frac{A}{1+AF} = \frac{\frac{1000}{1+j\omega/10^7}}{1 + \frac{1000 \cdot 0.05}{j\omega/10^7 \cdot j\omega/10^7}}$$

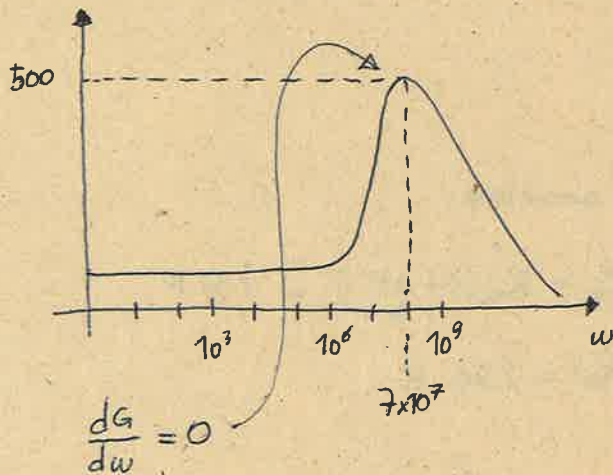
$$G(\omega)_F = \frac{10^{17}(1+j\omega/10^7)}{5.1 \times 10^{15} - \omega^2 + 2 \times 10^7 j\omega}$$




ω	0	10^6	10^7	40×10^7	7×10^7	8×10^7	10^8
$ G $	19.6	19.7	28.3	115	500	390	190

they can be exam questions!


10

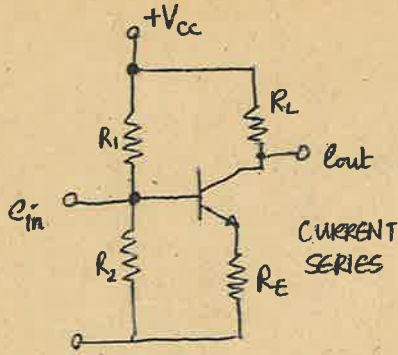


CURRENT SERIES

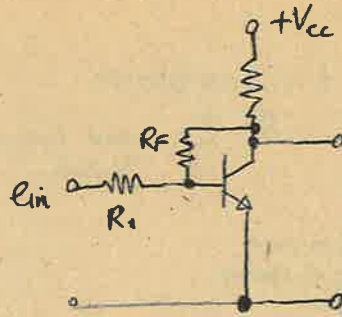

VOLTAGE SHUNT

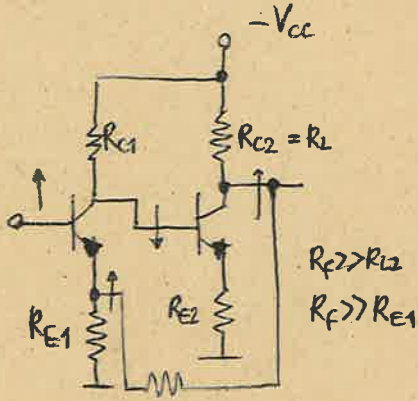


VOLTAGE SERIES

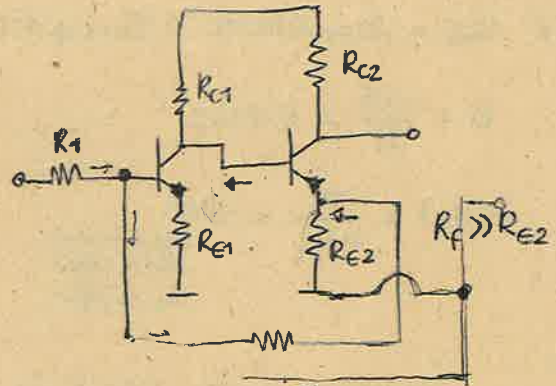

CURRENT SHUNT

11

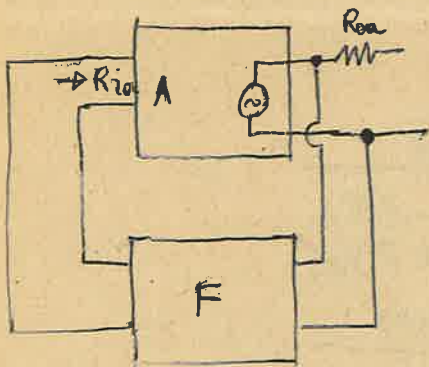

$$R_{in} = \frac{e_{in}}{i_{in}} = R_{ia}(1+AF) = 6K$$

$$R_{out} = \frac{e_{out}}{i_{out}} = R_{oa} \frac{1}{1+AF} = 333 \Omega$$

⇒ shunt olurlarda impedans düşer
series " " " yükselebilir

12 $R_{in} = \frac{R_{ia}}{1+AF} = 19.6 \Omega$

$R_{out} = \frac{R_{oa}}{1+AF} = 39.2 \Omega$

13 current series

$R_{in} = R_{ia}(1+AF) = 1.12K$

$R_{out} = 2.24K$

gain of the transimpedance amplifier:

$$G = \frac{-|A_{vi}|}{1 + \frac{R_{ia} + |A_{vi}|}{R_F}}$$

voltage gain of the transimpedance amplifier:

$$\frac{e_{out}}{e_{in}} = G = \frac{-|A| + \frac{R_{oa}}{R_F}}{1 + \frac{R_1}{R_{ia}} + \frac{R_{oa}}{R_L} + \frac{R_{oa}}{R_F} + \frac{R_1 R_{oa}}{R_F R_L} + \frac{R_1 R_{oa}}{R_{ia} R_L} + \frac{R_1 R_{oa}}{R_{ia} R_F} + \frac{R_1}{R_F} (1 + |A|)}$$

- 6.27 -

Simplified version of 6.27: $R_{oa} \ll R_F$
 $R_{oa} \ll R_L$

$$G = \frac{-|A|}{1 + \frac{R_1}{R_{ia}} + \frac{R_1}{R_F} (1 + |A|)}$$

and then if $R_1 < R_{ia} \Rightarrow G = \frac{-|A|}{1 + \frac{R_1}{R_F} (1 + |A|)}$

with some operations:


$$G = \frac{R_F}{R_1 + R_F} \frac{-|A|}{1 + |A| \frac{R_1}{R_F + R_1}}$$

↑
Feedback ratio

$$G \approx \frac{R_F}{R_1}$$

Derivations are not asked!

Introduction to operational amplifiers:

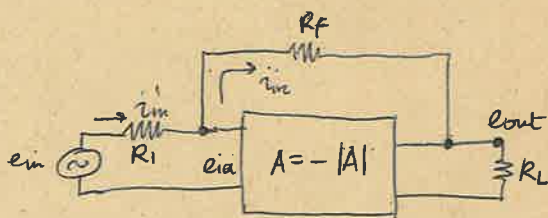


$$z_{in} = z_f = \frac{e_{in} - e_{out}}{R_1 + R_F}$$


$$e_{ia} = e_{in} = \frac{e_{in} - e_{out}}{R_1 + R_F} R_1 = e_{in} \frac{R_F}{R_1 + R_F} + e_{out} \frac{R_1}{R_1 + R_F}$$

superposition

Reflected resistance

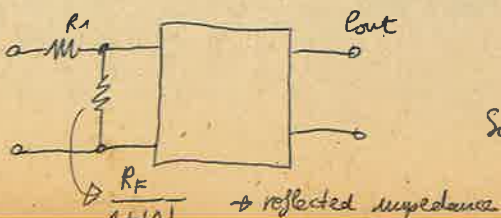


$$\text{So } G = -|A| \frac{R_{refl}}{R_1 + R_{refl}}$$

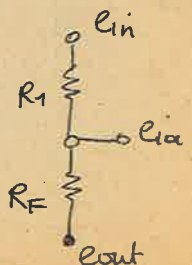


OPERATIONAL AMPLIFIERS!

$$G \approx -\frac{R_F}{R_1} \frac{1}{1 + j\omega/\omega_2 (1 + A_{MB}F)}$$

2JUN80

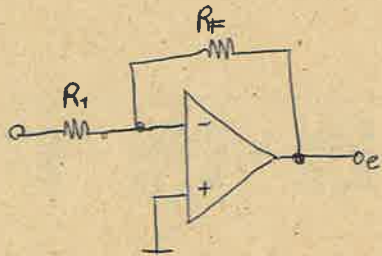

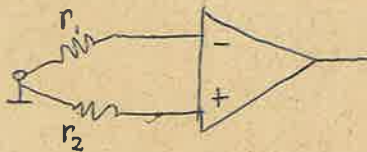
$$G = \frac{A}{1 + AF} \frac{R_F}{R_1 + R_F} \approx \frac{R_F}{R_1}$$



$$r_{in} = \frac{r_1 r_2}{r_1 + r_2}$$

6-14

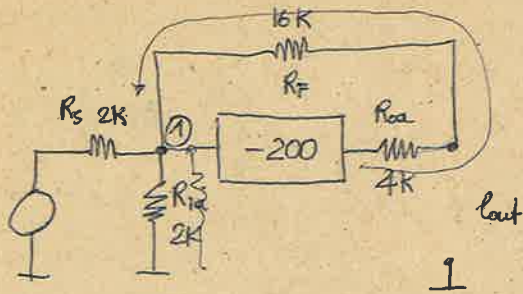

voltage - shunt. (operational amplifier)

using eq 6.27. $\approx -7.23 = G$

$$R_{in} = R_{1a} \parallel R_{ref} = 95.2 \Omega$$

$$R_{ref} = \frac{R_F + R_{oa}}{1 + |A|} = 0.1 \text{ k}$$

$$R_{out} = \frac{R_{oa}}{1 + AF} = 313.4 \Omega$$

200 1/17

$$F = \frac{R_s \parallel R_{1a}}{R_s \parallel R_{1a} + R_F} = \frac{1}{17}$$

6-15

$$R_F = 10K \quad G = 1.89$$

$$R_s = 5K \quad R_{in} = 67 \text{ at } 1$$

$$R_{out} = 154$$


6.16

$$G = -8.88$$

$$R_{in} = 113$$

$$R_{out} = 380$$

6-17

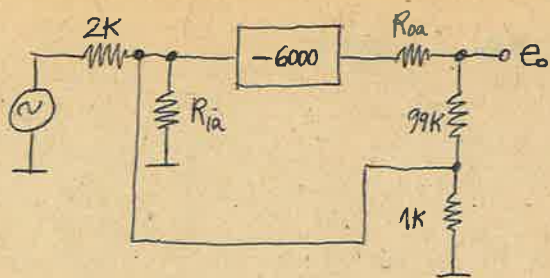

$$G = \frac{R_{refl}}{R_i + R_{refl}} |A|$$

$$R_{refl} = \frac{R_F}{1+6000} = 16.5 \Omega$$

$$G = \frac{16.5}{2k + 16.5} (-6000) = -49.7$$

$$R_{in} = 2016.5$$

6-18

$$R_{refl} = 165 \Omega$$

$$G = 45.7$$

$$R_{in} = 2165$$

6-19

$$G = \frac{R_{eq}}{R_{eq} + 2000} A = -49$$

$$R_{in} = R_1 + R_{eq} = 2016.45 \Omega$$

6-20

$$R_{oa} = 6k \quad 6.20 \text{ similar to } 6.14$$

$$\text{Using eq 6.27: } G = -47.6$$

$$R_{in} = R_1 + \left[R_{ia} \parallel \frac{R_F + R_{oa}}{1+A} \right]$$

0.86

1+A

since $R_L = 0$ reflected impedance can be considered $R_F + R_{oa}$ transferred.

$$R_{in} = 2.145 k$$

$$R_{out} = \frac{R_{oa}}{1+AF} = 161.5 \Omega$$

$$A = 6000$$

$$F = \frac{2k \parallel 0.86k}{99k + 2k \parallel 0.86k} = 0.00604$$

6-21

voltage shunt

5JUN80

Kitapları ~~örnek~~ örnek gelebilir (Ch 13) ^{ve} ~~Prb~~ Prb 123

'slow rate' can be asked in the exam.

"Nyquist formulation"

7JUN80

6.21

$$R_{ia} = 10k \parallel 80k \parallel (200 + 1 \times 26)$$

$$= 1.83 k \quad (\text{in the book: } 1.58 k)$$

$$r_H = \frac{26}{1} = 26 \Omega$$

from equation 6.27.
 $R_L = \infty$
 $R_{oa} = \text{small}$

$$G = \frac{-|A|}{1 + \frac{R_1}{R_{ia}} + \frac{R_1}{R_F} (1+A)}$$

A: unloaded open-loop gain

$$A = A_{bc1} \frac{R_{in2}}{R_{in2} + R_{c1}}$$

$$171.886$$

$$\rightarrow 4k \parallel (R_F + 0.5 \parallel 1.83)$$

$$G = 7.67 \quad (7.65 \text{ in the book})$$

$$A = \frac{\beta R_{c1}}{r'_{bb} + (1+\beta)r_d} \times \frac{r'_{bb} + (1+\beta)r_d + (1+\beta) \left[\frac{4k \parallel (R_F + 0.5 \parallel 1.83)}{\beta + 171.886} \right]}{\beta + 171.886}$$

$$A = 265.2 \quad (252 \text{ in the book})$$


$$R_{in} = R_{ia} \parallel R_{refl} = R_{ia} \parallel \frac{R_F}{1+A} = 14.9 \Omega$$

266

6.22 : $R_F = 10K$
 $R_{ia} = 1.83K$
 $A = -268.8$
 $G = -18.27$
 $R_{in} = 36.46 \Omega$

6.23 $R_{ia} = 1.83K$
 $G = A$
 $R_{in} = R_{ia} // R_F = 1.255K$

6.24

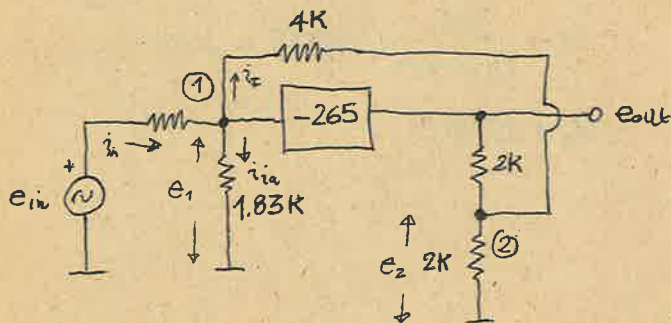

at node 1 $\frac{e_{in} - e_1}{0.5} = \frac{e_1 - e_2}{4K} + \frac{e_1}{1.83}$


at node 2 $\frac{e_2}{2K} = \frac{e_{out} - e_2}{2K} + \frac{e_1 - e_2}{4K}$

four equations
with four unknowns

$G = \frac{-265}{14.623} = -18.1$

3) $e_{out} = -265 e_1$

4) $\frac{e_{out}}{e_{in}} = G$

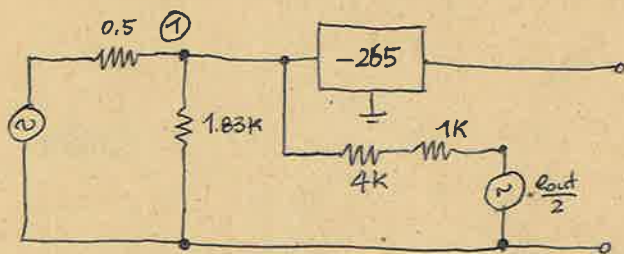


$R_{in} \text{ at } \textcircled{1} = 36.7 \Omega$

In order to continue the process of manufacturing

Rule I $AR \geq AVC$
must be

Total profit : Total revenue - total cost

6-25

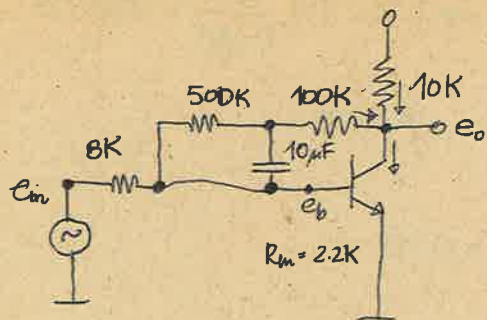

current eq:

$$\frac{e_{in} - e_b}{8K} = \frac{e_b}{R_{ia}} + \frac{e_b - e_{out}}{R}$$

$$R \begin{cases} R_{DC} = 600K \\ R_{AC} = 100K \end{cases}$$

$$\frac{e_{out}}{10} + 100 \frac{e_b}{2.2} = \frac{e_b - e_{out}}{R}$$

$$G_{DC} = \left. \frac{e_{out}}{e_{in}} \right|_{dc} = -42.135$$

$R_{DC} = 600K$

$$G_{AC} = \left. \frac{e_{out}}{e_{in}} \right|_{ac} = -10.939$$

$R_{AC} = 100K$

6.26 in the book

- CHAPTER 13 -

13.1

$m = 5$
 $V_0 = -10V$
 $V_1 = +6V$

$$CF = \frac{V_0}{2^m - 1}$$

conversion factor

general

$$CF = \frac{R_F}{R_A} V_1$$


binary weighted resistors

$$CF = \frac{R_F}{2^m R} V_{REF}$$

ladder network

$$\frac{R_F}{R_A} V_1 = \frac{V_0}{2^m - 1}$$
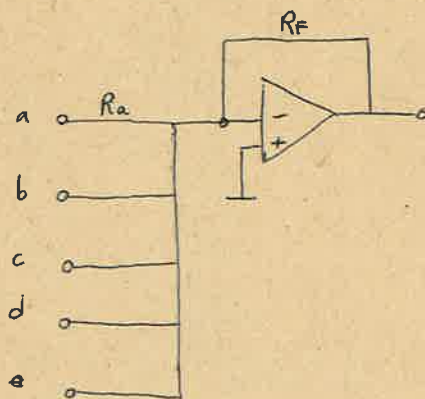
$$\frac{R_F}{R_A} = \frac{V_0}{V_1} \frac{1}{2^m - 1} = \frac{10}{6} \frac{1}{31} = 0.053$$



13.2 (The answer given in the book is WRONG)

$$V_o = -8$$


$$CF = .058$$

$$V_i = +6$$

$$CF = \frac{V_o}{2^m - 1}$$


$$2^m - 1 = \frac{V_o}{CF} \Rightarrow 2^m = 1 + \frac{8}{0.058} = 138.93$$

$$m = 7$$

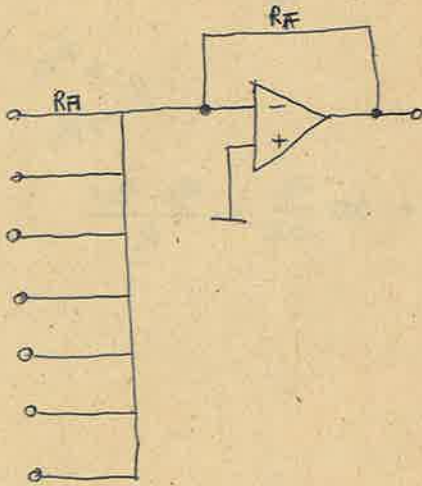

$$\frac{R_F}{R_A} = \frac{0.058}{6} = 0.097$$


13.3

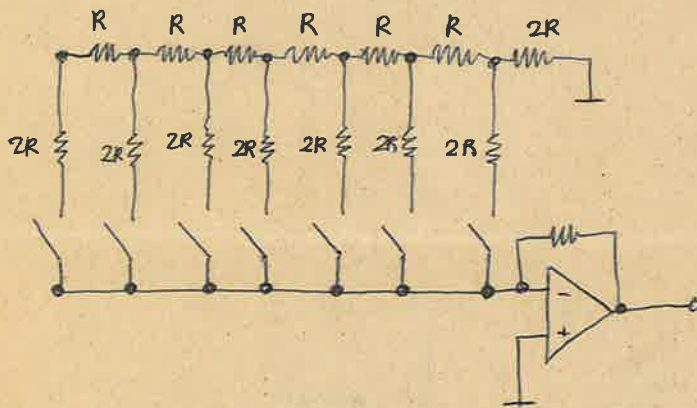

$$0.058 = \frac{R_F}{R} \frac{6}{128}$$

$$\frac{R_F}{R} = \underline{\underline{1.237}}$$

- TRANSISTOR AT HIGH FREQUENCY -

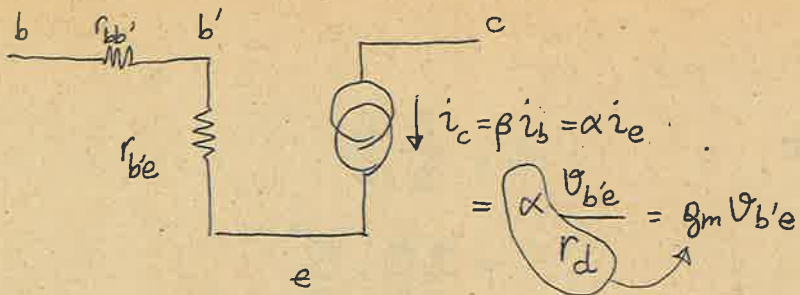

$$g_m = \frac{i_{out}}{V_{in}}$$



$$r_c = g_m V_{b'e}$$

$$g_m r_d = \alpha$$

$$g_m r_{be} = \beta$$

$$g_m R_L = A$$

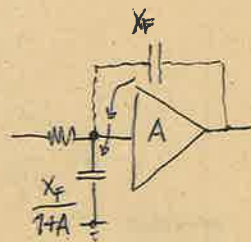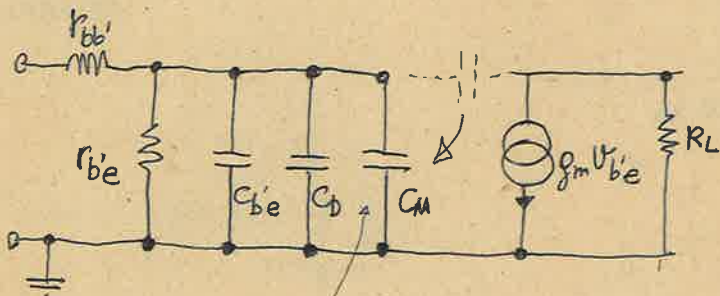tubes $g_m r_p$
 -transist. $g_m r_c$
 FET $g_m r_{ds}$ } μ



$$|X_F| = \frac{1}{\omega C_{b'e}}$$

$$X_{refl} = \frac{1/\omega C_{b'e}}{1+A} = \frac{1}{\omega C_{b'e} (1+A)}$$


transistor's

$$A = g_m R_L = \frac{\alpha}{r_d} R_L$$

$$C_M = C_{bc} \left(1 + \alpha \frac{R_L}{r_d} \right)$$

PROB 7-1

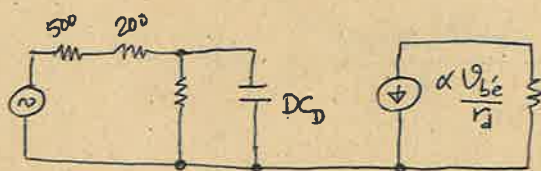- $\alpha = 0.99$
- $r_{bb'} = 200 \Omega$
- $C_{bc} = 5 \text{ pF}$
- $f_T = 10 \text{ MHz}$
- $R_L = 1 \text{ K}$
- $I_E = 1 \text{ mA}$
- $R_S = 500 \Omega$



$$\beta = \frac{\alpha}{1-\alpha} = 99$$

$$A_{MB} = \frac{\beta R_L}{R_S + r_{bb'} + r_{be}} = \frac{-99 \times 10^3}{500 + 200 + 2600} = -30$$

$A_{MB} = ?$
 $f_2 = ? = \frac{B}{D} f\beta$

$$A_v = A_{MB} \left(\frac{1}{1 + j\omega/\omega_2} \right)$$

$$B = \frac{R_s + r_{bb'} + r_{b'e}}{r_{bb'} + r_{b'e}} = \frac{3300}{700} = 4.71$$

$$D = 1 + \alpha R_L C_{bc} \omega_t$$

$$= 1 + 0.99 \times 10^3 \times 5 \times 10^{-12} \times 10^7 \times 2\pi$$

$$= 1.31$$

$$f_2 = \frac{B}{D} \frac{f_t}{\beta}$$

$$= \frac{4.71}{1.31} \times \frac{10^7}{99}$$


$$= 360 \text{ kHz}$$

16J80

Tuned Amplifiers


Problem

There are two stations:

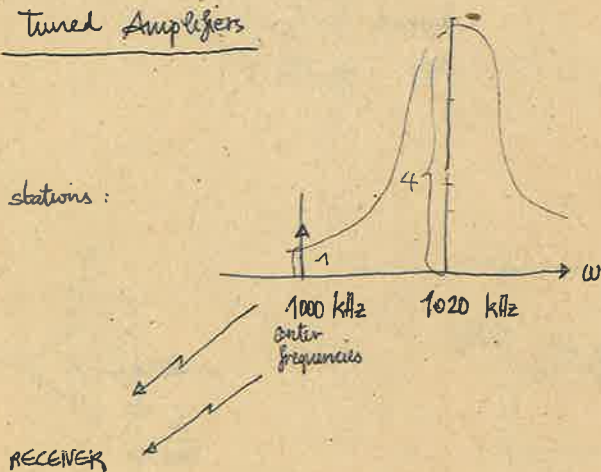

$$\frac{V}{V_0} = \frac{1}{4} \text{ given}$$

19JUN80

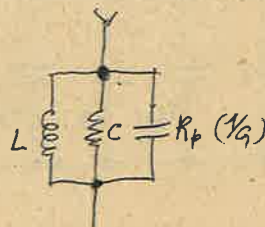

a) determine the values: G, C

$$L = 50 \mu\text{H}$$

b) What is the bandwidth?

Answer

a) $f_0 = 1000 \text{ kHz} = 10^6 \text{ Hz}$

$$\omega_0 = 2\pi \times 10^6 \text{ rad/sec} = \frac{1}{\sqrt{LC}} \Rightarrow C = 507 \times 10^{-12} \text{ F}$$

$$\boxed{507 \text{ pF}}$$

b) $\frac{V}{V_0} = \frac{1}{4} = \left| \frac{1}{1 + j2\delta Q} \right| = \frac{1}{\sqrt{1 + 4\delta^2 Q^2}}$

$$\delta Q = 1.94$$

$$\delta = \frac{\omega - \omega_0}{\omega_0} = \frac{1020 - 1000}{1000} = \frac{20}{1000} \quad \delta = 0.02$$

$$Q = \frac{1.94}{\delta} \Rightarrow Q = 97$$

$$Q_p = \frac{\omega_0 C}{G} = \frac{2\pi \times 10^6 \times 507 \times 10^{-12}}{G} = 97$$

$$\boxed{G = 32 \times 10^{-6} \text{ S}}$$

$$\text{BW} = \omega_2 - \omega_1 = \frac{\omega_0}{Q} = \frac{2\pi \times 10^6}{97} = 64.8 \times 10^3 \text{ rad/sec}$$

half power frequencies

$$\boxed{\text{BW} = 10.3 \text{ kHz}}$$

- MODIFIED RESONANCE CCT -

$$Z_0 = \frac{L}{RC} = R_p$$



Example (from Comar)

Given

$$\begin{cases} R_s + r_{bb'} + r_{b'e} = 3 \text{ k}\Omega \\ \beta = 100 \\ \omega_0 = 6.28 \times 10^5 \text{ rad/sec} \\ L = 1 \text{ mH} \\ Q_{\text{eff}} = 50 \end{cases}$$


$$A = \frac{-\beta R_{sh}}{R_s + r_{bb'} + r_{b'e}} = \frac{-\beta \omega_0 L Q_{\text{eff}}}{R_s + r_{bb'} + r_{b'e}}$$

$$A = \frac{-100 \times 6.28 \times 10^5 \times 10^{-3} \times 50}{3000} \approx -10000$$

$$BW = \frac{f_0}{Q_0} \rightarrow \frac{f_0}{Q_{\text{eff}}} = \frac{100 \times 10^2}{50} = 2000 \text{ kHz}$$

23.6.80

High frequency considerations in FET

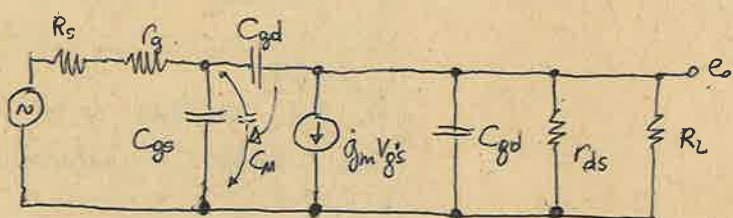

$$C_M = C_{gd} (1 + g_m R_{eq})$$

$$R_{eq} = R_L \parallel r_{ds}$$

$$C_{ds} \approx C_{gs} > C_{gd}$$

5 pF 0.5 pF

$$C_{in} = C_{gs} + C_M$$

corners due to time constants

$$\omega_1 = \omega_{in} = \frac{1}{\tau_{in}} = \frac{1}{(R_s + r_g) C_{in}} \approx \frac{1}{R_s C_{in}}$$


$$\omega_2 = \omega_{out} = \frac{1}{\tau_{out}} = \frac{1}{R_{eq} C_{ds}} \approx \frac{1}{R_L C_{ds}}$$

GBW considerations


$$GBW = A_{MB} \omega_2 = \frac{\omega_x}{D} \frac{\beta R_c}{R_s + r_{bb'}}$$

for GBW to be constant

Box compensation

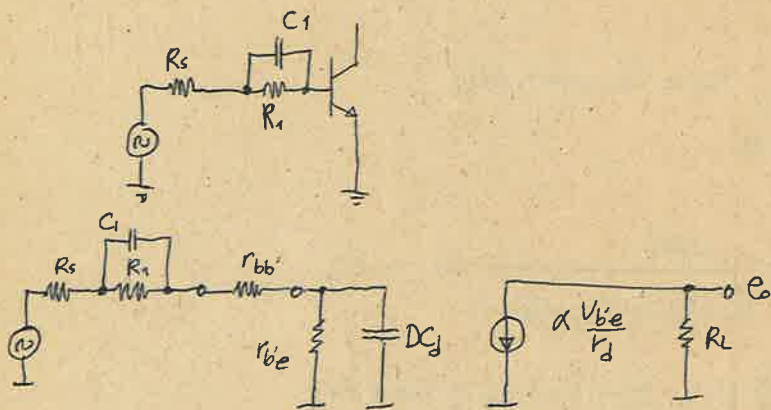

Simplifying:

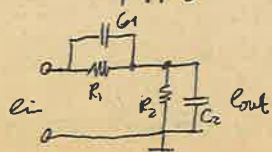

must be:

$$R_1 C_1 = R_2 C_2$$

then the network becomes frequency independent:

$$\frac{e_{out}}{e_{in}} = \frac{R_2}{R_1 + R_2}$$

Emitter compensation


Case I



Case II


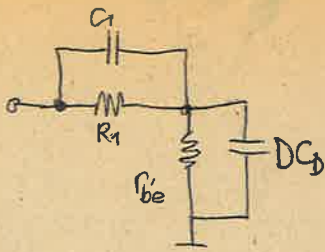
$$\frac{e_{out}}{e_{in}} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2}{1 + j\omega C_2 R_2} + \frac{R_1}{1 + j\omega C_1 R_1}$$



$Z_1 = Z_2$
 $R_1 C_1 = DC_b r'_{be} \left(\frac{1}{\omega \beta} \right)$
 $C_1 = \frac{DC_b r'_{be}}{R_1} = \frac{D}{R_1 \omega \beta}$

ITERATIVE STAGES

$\omega_{20} = \omega_2 \sqrt{2^{1/n} - 1}$ bandwidth shrinkage equation

$\sqrt{2^{1/n} - 1} \approx \frac{1}{1.2\sqrt{n}} \quad n \geq 3$

$\omega_{20} = \frac{\omega_2}{1.2\sqrt{n}}$

CH 7

7.1 - 7.3A (270 - 335)

7.4 tuned stages ABCDE (319 - 327)

CH 12

the first 36 Pages, up to Class C amplifiers (not included)

CH 8


8.2 SCR (366 - 375)

CH 15

15.4 (674 - 678)

Vacuum tubes: Angelo 307 - 318

Example (From Camer)

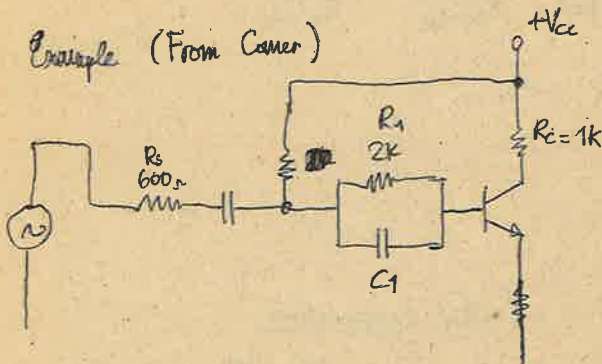

- $f_t = 100 \text{ MHz}$
- $\beta = 100$
- $r'_{bb'} = 100 \Omega$
- $r_d = 13 \Omega$
- $C_{bc} = 5 \text{ pF}$ (at bias point)
- $A_{MB} = ?$
- $f_n = ?$

- a) $R_1 = 2k, C_1 = \text{the correct value}$
- b) $R_1 = C_1 = 0$

a) $A_{MB} = \frac{-\beta R_L}{R_s + r'_{bb'} + r'_{be} + R_1} = -25$

$f_2 = \frac{f_p}{D} B = \frac{f_p}{D} \left(\frac{R_s + r'_{bb'} + r'_{be} + R_1}{R_s + r'_{bb'}} \right)$

$f_p = \frac{f_t}{\beta} = \frac{100 \text{ MHz}}{100} = 1 \text{ MHz}$

~~XXXXXXXXXX~~ $D = 1 + \alpha R_L \omega C_{bc} = 1 + 0.99 \times 10^3 \times 2\pi \times 10^8 \times 5 \times 10^{-12} = 4.1$

$$f_2 = \frac{1 \text{ MHz}}{4.1} \times \frac{4013}{700} = 1.4 \text{ MHz}$$

$$C_1 = \frac{D}{R_1 \omega_3} = \frac{4.1}{2 \times 10^3 \times 2\pi \times 10^6} = \underline{302 \times 10^{-12} \text{ F}}$$

b) $f_2 = \frac{f\beta}{D} B$

$$B = \frac{2013}{700} = 2.88$$

$$f_2 = \frac{1}{4.1} \times 2.88 = 0.7 \text{ MHz}$$

$$A_{MB} = -50 \text{ ?}$$

7.3


$n = 13.8$ $\rightarrow n = 2 \ln A_{MB0}$
must be integer
14 nearest higher integer

POWER AMPLIFIERS

30680

Power hyperbola

$P = \theta T = \text{constant}$

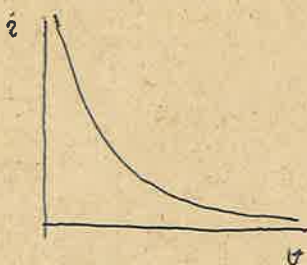

3780

Thermal equilibrium criteria :

$$\frac{1}{\theta} \geq \frac{P}{T} \quad \text{power dissipated}$$

$$\underline{7.1} \quad C = \frac{k}{\sqrt{\phi - V}}$$

$$C = 10 \text{ pF}$$

$$V = -6 \text{ V}$$

$$\phi = 0.7$$

find C for 12 V reverse bias.


7.2

Similar to 7.1

7.5

$$\omega_p = \frac{1}{(1+\beta)r_d C_D} \Rightarrow C_D = \frac{1}{(1+\beta)r_d \omega_p}$$

* 7.7

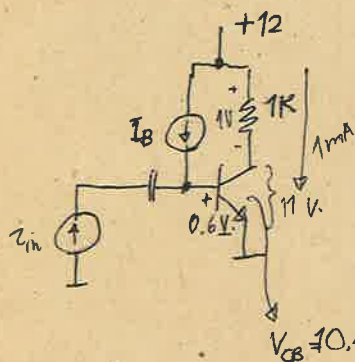

$$\omega_2 = \omega_\beta \frac{B}{D} \quad B \rightarrow 1$$

$$\omega_2 = \frac{\omega_t}{\beta} \frac{1}{D}$$

$$D = (1 + \alpha R_L C_{bc} \omega_t)$$

$$V_{CB} = 10.4 \text{ V}$$

$$\omega_t = 6.28 \times 10^6 \text{ rad/sec}$$

$$\beta = 70$$

$$C_{bc} = 20 \text{ pF}$$

$$V_{CB} = 6 \text{ V}$$

$$\phi = 0.8 \text{ V}$$

$$\left. \frac{i_{out}}{i_{in}} \right|_{I_E = 1 \text{ mA}}$$

$$C_{bc} \Big|_{V=10.4} = 15.6 \text{ pF}$$

$$D = (1 + \frac{70}{71} 1000 \times 15.6 \times 10^{-12} \times 6.28 \times 10^6) = 1.10$$

$$\omega_2 = \frac{6.28 \times 10^6}{70 \times 1.10} = 81.8 \times 10^3 \text{ rad/sec.}$$

7.8 similar to 7.7 $R_s \rightarrow \infty \Rightarrow \beta = 1$

$$I_C \approx I_E = 1 \text{ mA}$$

$$V_{CE} = 12 - 4 = 8 \text{ V}$$

$$V_{BC} = 8 - 0.6 = 7.4 \rightarrow C_{bc} = 18.2 \text{ pF}$$

$$D = 1.11$$

$$\omega_2 = \frac{6.28 \times 10^6}{70 \times 1.11} = 80.6 \times 10^3 \text{ rad/sec}$$

* 7.11

$$A_{vB} = \frac{\beta R_c}{R_s + r_{bb'} + r_{b'e}} = \frac{100 \times 1000}{600 + 100 + 1030} = -57.8$$

$$I_E = \frac{(E_{th} - 0.6)(1+\beta)}{R_{th} + (1+\beta)R_E}$$

$$f_2 = f_\beta \frac{B}{D}$$

$$B = \frac{R_s + r_{bb'} + r_{b'e}}{R_s + r_{bb'}} = 2.47$$

$$r_{b'e} = (1+\beta)r_d$$

$$D = 1 + \frac{100}{101} \times 10^3 \times 2 \times 10^{-7} \times 10^{-11}$$

$$D = 1.628$$

$$E_{th} = \frac{8}{8+62} \cdot 18 = 2.06 \text{ V}$$

$$\frac{f_t}{\beta}$$

$$R_{th} = \frac{62 \times 8}{62+8} = 7.09 \text{ k}$$

$$f_2 = \frac{10^7}{100} \frac{2.47}{1.628} = 153.2 \text{ kHz.}$$

$$I_E = 2.56 \text{ mA}$$

$$r_d = \frac{26}{2.56} = 10.2 \Omega$$

7.12 Same equations used in 7.11

Explanation: $f_2 = f_\beta \frac{B}{D} = \frac{f_t}{\beta} \frac{B}{D}$

$\rightarrow 1 + \alpha R_L C_{bc} 2\pi f t$
D is increased too.

7.13 Equations used in 7.11

7.14 " " " "

7.15 " " " " 7.12

7.18 7.11, 7.12

7.19 $A_{MB} = -g_m (r_{ds} \parallel R_L)$

$C_{in} = C_{gs} + (1 + A_{MB}) C_{gd}$

$f_2 = \frac{1}{2\pi R_s C_{in}}$

$A = \frac{-g_m R_{eq}}{(1 + j\omega R_s C_{in})(1 + j\omega R_{eq} C_{ds})}$

$R_{eq} = \frac{r_{ds} R_L}{r_{ds} + R_L}$

$R_s \text{ large} \Rightarrow f_2 = \frac{1}{2\pi R_s C_{in}}$

$A_{MB} = -6000 \times 10^{-6} \frac{100 \times 2}{100 + 2} \text{ k}\Omega = -11.8$

$C_{in} = 3.5 + (11.8) 3 = 41.8 \text{ pF}$

$f_2 = \frac{1}{2\pi 20000 \times 41.8 \times 10^{-12}} = 190 \text{ kHz}$

7.20

7.21 Same equations as 7.19

7.22

7.23

$GBW = |A_{MB}| \times \omega_2 = 20 \times 2\pi \times 560 \times 10^3 = 7.03 \times 10^7$

$GBW = \frac{\omega_c \beta R_L}{D (r_{bb'} + R_s)} = \frac{\omega_c R_L}{D (r_{bb'} + R_s)} = \frac{2\pi \times 10^7 \times R_L}{1 + \frac{99}{100} \times R_L \times 2\pi \times 10^7 \times 8 \times 10^{-12}}$

(0.1 + 0.2)

Solve for R_L

$R_L = 0.33642 \text{ K}$

find D: $D = 1 + \alpha R_L \omega_c C_{bc}$

$D = 1.1674$

$\omega_2 = \frac{\omega_B}{D} \times B = \frac{2\pi \times 10^7}{99 \times 1.1674} \times B = 2\pi \times 560 \times 10^3$

Solve for B

$B = 6.472$

$B = \frac{R_s + r_{bb'} + r_{b'e}}{R_s + r_{bb'}}$

$r_{b'e} = 1.642 \text{ K}$

7.24 $GBW = \frac{\omega_c}{D} \frac{R_L}{r_{bb'} + R_s}$

$GBW = \frac{2\pi \times 10^7}{D} \frac{200}{100 + 200} = 3.81 \times 10^7$

$D = 1 + \alpha R_L \omega_c C_{bc} 8 \times 10^{-12}$
 $= 1.09952$

$A_{MB} = \frac{GBW}{\omega_2} = \frac{3.81 \times 10^7}{2\pi \times 10^6} = 6.064$

7.25 $R_1 C_1 = r_{be} D C_D = \frac{D}{\omega \beta}$

$C_1 = \frac{D}{R_1 \omega \beta} = \frac{1.628}{3 \times 10^3 \times \frac{10^7}{100} \times 2\pi} = 0.086 \times 10^{-8}$

$C_1 = 863.7 \text{ pF}$

$A_{MB} = - \frac{\beta R_L}{R_S + R_1 + r_{bb'} + r_{be}} = - \frac{100}{4.73}$


$A_{MB} = -21.14$

$f_2 = f_p \frac{B}{D} = \frac{1 \times 10^5}{1.628} \frac{R_S + R_1 + r_{bb'} + r_{be}}{R_S + r_{bb'}}$

$f_2 = 415 \text{ kHz}$

7.26 Similar to 7.25

7.27 (Fig 7.19)

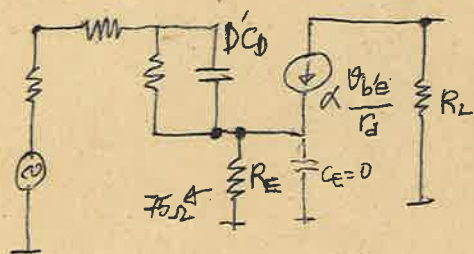

$\beta = 100$
 $r_{bb'} = 100 \Omega$
 $V_{BE} = 0.6 \text{ V}$
 $f_T = 10^7 \text{ Hz}$
 $C_{be} = 10 \text{ pF}$
 $R_S = 600 \Omega$

$i_E = 4 \text{ mA}$
 $A_{MB} = - \frac{\beta R_L}{R_S + r_{bb'} + r_{be} + (1 + \beta) R_E} = -11.173$


$f_2 = \frac{26}{4} = 6.5 \Omega$

$r_{be} = 101 \times 6.5 = 656.5 \Omega$

$f_2 = f_p \frac{B}{D'}$

$= \frac{10^7}{100} \frac{R_S + r_{bb'} + r_{be} + (1 + \beta) R_E}{1 + (\alpha R_L + r_d + R_E) \omega C_{be}} \times \frac{R_S + r_{bb'} + r_{be} + (1 + \beta) R_E}{R_S + r_{bb'} + R_E} = \frac{10^7}{100} \times 6.965$


$f_2 = 696.5 \text{ kHz}$

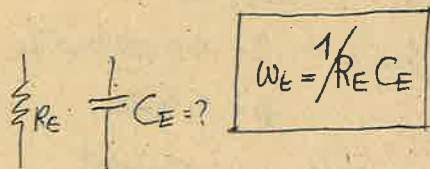

$C_E = \frac{1}{R_E \omega} = \frac{1}{75 \times 2\pi \times 696.5 \times 10^3} = 212.21 \times 10^{-12}$


7.28 - 7.29 - 7.30 → 7.27

7.31

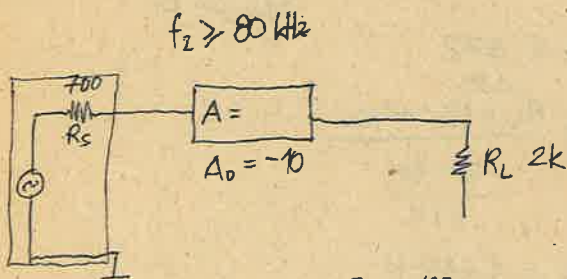

$10 = |A_{MB}| = \frac{\beta R_L}{R_S + r_{bb'} + (1 + \beta) r_d} \Rightarrow r_d = 190 \Omega$

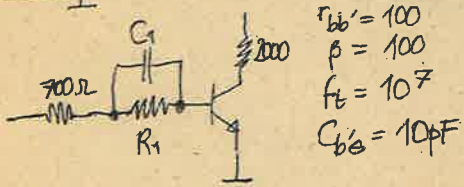$I_E = \frac{26}{190} = 0.137 \text{ mA}$



$r_{bb'} = 100$
 $\beta = 100$
 $f_T = 10^7$
 $C_{be} = 10 \text{ pF}$

$f_2 = f_p \frac{B}{D} \geq 80 \times 10^3 \text{ Hz}$

$= \frac{10^7}{100} \frac{B}{D} \geq 80 \times 10^3$

$\frac{B}{D} \geq 0.8$

$$|A_{MB}| = \frac{\beta R_L}{R_s + r_{bb'} + R_1 + r_{be}} = 10$$

$$r_{be} + R_1 = 19.2 \times 10^3$$

$$\frac{B}{D} = \frac{R_1 + R_s + r_{bb'} + r_{be}}{R_s + r_{bb'}} \geq 0.8$$

$$1 + \alpha R_L \omega_t C_{b'e}$$

$$R_1 + r_{be} \geq 636.2$$

(CONTINUED)

7.33

$$A_{MB} = \frac{-\beta R_c}{R_s + r_{bb'} + r_{be} + (1+\beta)R_E}$$

↑ assumption needed.

eg. $I_E = 4 \text{ mA}$

$$r_{be} = 656.7 \Omega$$

$$f_2 = f_3 \frac{B}{D'}$$

$$B = \frac{R_s + r_{bb'} + r_{be} + (1+\beta)R_E}{R_s + r_{bb'} + R_E}$$

⇒ R_E

$$C_E = \frac{1}{R_E \omega_t}$$

$$\omega_2 = \omega_B \frac{B}{D'}$$

$$f_2 = f_3 \frac{B}{D'}$$

can be asked.

7.35 See 7.11

$$GBW = \frac{\omega_t}{D} \frac{R_L}{r_{bb'} + R_s} \quad ; \quad A_{MB}$$

$$\omega_2 = \frac{GBW}{A_{MB}}$$

7.36 Same as 7.35

except D' instead of D

7.37

$$A_0 = \frac{A_{MB}}{\left(1 + j \frac{f}{f_{21}}\right) \left(1 + j \frac{f}{f_{22}}\right) \left(1 + j \frac{f}{f_{23}}\right)}$$

\uparrow \uparrow \uparrow
 1 MHz 2 MHz 10 MHz

$$\left[1 + \left(\frac{f}{1}\right)^2\right] \left[1 + \left(\frac{f}{2}\right)^2\right] \left[1 + \left(\frac{f}{10}\right)^2\right] = 2$$

$$f = 832 \text{ kHz}$$

7.38 Same with 7.37

Answer: 595 kHz.

can be asked.

7.39 $f_{20} = 3.1 \text{ MHz}$



$$GBW = 1 \times 10^8 \text{ rad/sec}$$

$$\frac{dW}{dn} = 0 \quad A_{MB} = 1.65$$

$$1 \times 10^8 \text{ GBW} = 1 \times 10^8 \text{ rad/sec}$$

$$\frac{(GBW)_n}{1.65} = \omega_2 = 60.606 \times 10^6 \text{ rad/sec}$$

$$w_{20} = w_2 \sqrt{2^{1/n} - 1}$$

$$3.1 = 9.65 \sqrt{2^{1/n} - 1}$$

$$n = 7.058$$

$$\boxed{n = 7}$$

$$\textcircled{*} \underline{7.49} \quad f_0 = \frac{1}{2\pi\sqrt{LC}} \rightarrow C$$

$$R_p = Q_0 \omega_0 L$$

$$R_{sh} = R_p \parallel R_1$$

$$Q_{eff} = \frac{R_{sh}}{\omega_0 L} = \frac{R_{sh}}{R_p} Q_0 \rightarrow \text{ANSWER}$$

$$BW = \frac{f_0}{Q_{eff}}$$

7.50 Same as 7.49.


$$\textcircled{*} \underline{7.51} \quad L = \frac{1}{\omega_0^2 C}$$

$$Q_{eff} = \frac{f_0}{BW} = \frac{R_{sh}}{\omega_0 L} \Rightarrow R_{sh}$$

$$R_{sh} = R_1 \parallel R_p \rightarrow R_p$$

12780

12-1

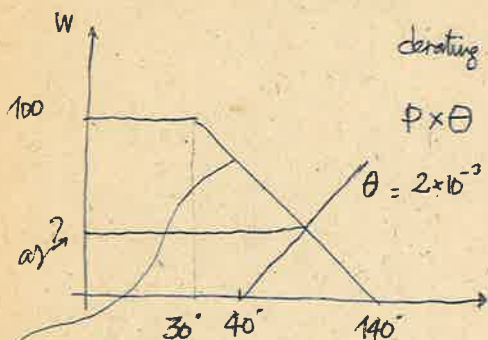

derating \equiv thermal conductance $= \frac{1}{\theta}$

$$P \times \theta = T_2 - T_1$$


$$\theta = 2 \times 10^{-3} \text{ } ^\circ\text{C}/\text{mW}$$

a) $\theta_{tot_a} = 2^\circ\text{C}/\text{W}$ $\theta_{tot} = \theta_i + \theta_{HS}$

$$\theta_{tot_b} = 4^\circ\text{C}/\text{W}$$

$$\theta_A = 10^\circ\text{C}/\text{W}$$
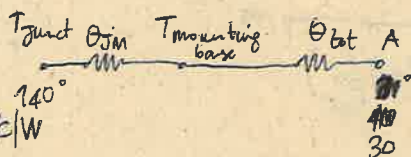
$$\theta_{JM} = \frac{T_2 - T_1}{P} = \frac{140}{100} = 1.4^\circ\text{C}/\text{W}$$



$$P_a = \frac{140 - 40}{3.1} = 32.25 \text{ W.}$$

$$P_b = \frac{140 - 40}{5.1} = 19.6 \text{ W.}$$

$$P_{o_{air}} = \frac{140 - 40}{11.1} = 9.01 \text{ W.}$$

12-2 a) $T_J \xrightarrow{1.1} \xrightarrow{2} T_A -20$

$$T_J - T_A = \frac{140 - (-20)}{1.1 + 2}$$

$$P_A = \frac{160}{3.1} = 51.6 \text{ W} \quad P_{\theta} = T$$

$$P_b = \frac{160}{5.1} = 31.37 \text{ W}$$

$$P_c = \frac{160}{11.1} = 14.4 \text{ W}$$

12-4

$$P = 20 \text{ W} = \frac{140 - 30}{1.1 + \theta_{TOT}}$$

$$\theta_T = \frac{110 - 22}{20} = 4.4 \text{ } ^\circ\text{C/W}$$

12-3

$$T_J - T_A = P\theta$$

\uparrow \uparrow \uparrow
 140 100 3.1



$$T_J - T_A = 100 \times 3.1 = 310$$

$$T_A = -310 + 140 = -170 \text{ } ^\circ\text{C}$$

12-5

$$P = 10 \text{ W} = \frac{140 - 30}{1.1 + \theta_c}$$
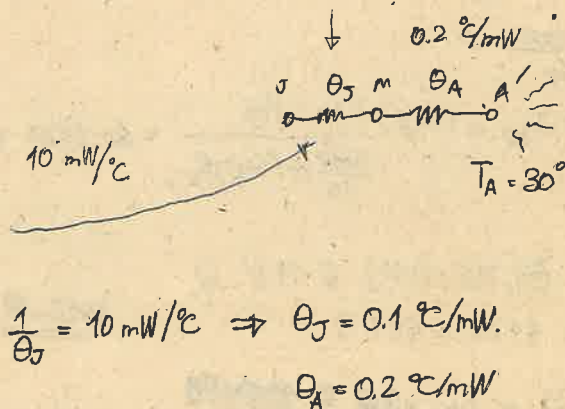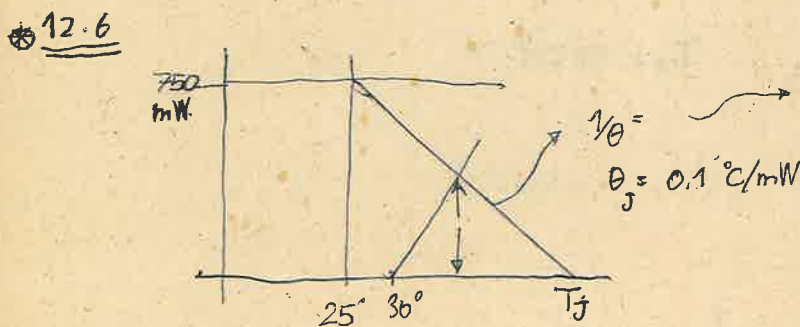
$$\theta = 9.9 \text{ } ^\circ\text{C/W}$$




$$T_J - 25 = 750 \times 0.1$$

$$T_J = 100$$

$$P = \frac{100 - 30}{0.1 + 0.2} = 233.3 \text{ ANSWER}$$

12.7 - 12.8 → 12.6

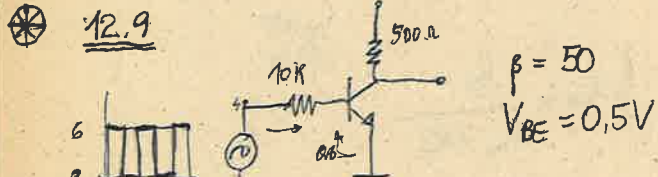

a) find P_T

b) $\theta_c = \theta_J + \theta_{HS} = ?$

$$\begin{cases} \theta_J = 0.1 \text{ } ^\circ\text{C/mW} \\ T_{J_{max}} = 100 \text{ } ^\circ\text{C} \\ T_A = 30 \text{ } ^\circ\text{C} \end{cases}$$


$$I_c = \beta I_B$$

$$I_B = \frac{6 - 0.6}{10K} = 0.54 \text{ mA}$$

$$I_c = 50 \times 0.54 = 27 \text{ mA}$$

$$I_B = \frac{2 - 0.6}{10K} = 0.14 \text{ mA}$$

$$I_c = 50 \times 0.14 = 7 \text{ mA}$$

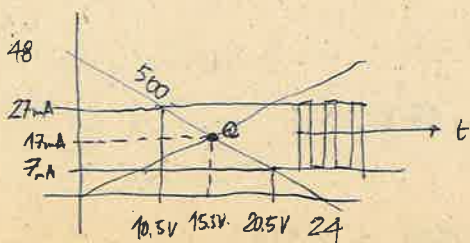

$$P_T = \frac{V_1 I_1 + V_2 I_2}{2} = \frac{10.5 \times 27 + 20.5 \times 7}{2} = 213.5 \text{ mW}$$

$$P_{out} = \frac{V}{2} \times (5 \times 10 \text{ mA}) = 100 \text{ mW}$$

$$P_T = P_{T_d} - P_{out} = 15.5 \times 17 - 100 = 213.5 \text{ mW}$$



100°C 0.1 $\theta_{\text{C}} = ?$
 $\rightarrow 213.5 \text{ mW}$

12-10, 11, 12, 13, 14 \rightarrow 12.9

$100 - 30 = 213.5(0.1 + \theta_{\text{C}})$

$\theta_{\text{C}} = 0.228 \text{ }^\circ\text{C/mW}$

12.15

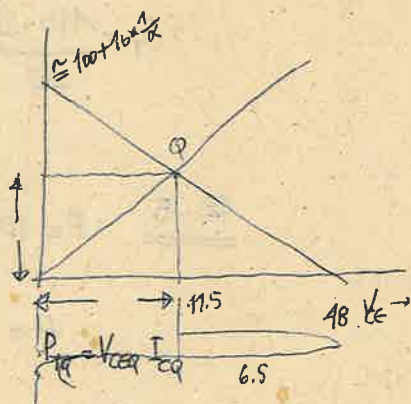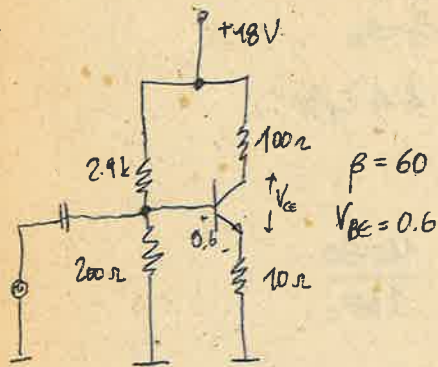

a) Find the Q point

$E_{\text{th}} = \frac{200}{2600} 18 = \frac{18}{13}$

$R_{\text{th}} = \frac{200 \times 2400}{2600} =$

$I_{\text{CQ}} = (1 + \beta) I_{\text{BQ}} = (1 + \beta) \frac{E_{\text{th}} - V_{\text{BE}}}{\frac{2400}{13} + (1 + \beta) R_{\text{E}}} = 60.2323 \text{ mA}$ $I_{\text{CQ}} = 59.245 \text{ mA}$

I_{CQ}

$V_{\text{CE}} = 18 - (59.245 \times 0.11) \approx 11.5 \text{ V}$

$P_{\text{TQ}} = 11.5 \times 59.26 = 681.3$

12-19

d) $P_{\text{S}} = I_{\text{DC}} 24 = I_{\text{CQ}} \times 24 = 1.4216 \text{ W}$
 $= 60.2323 \times 18$
 $= 1.0842 \text{ W}$


b) ~~1.0842 W~~

$P_{\text{ac}} = \frac{1}{2} \frac{(5.92)^2}{100} = 175 \text{ mW}$

$P_{\text{ac}} = \frac{1}{10} P_{\text{ac}} = 17.5 \text{ mW}$

$P_{\text{ac}}(\text{tot}) = 175 + 17.5 = 192.5$

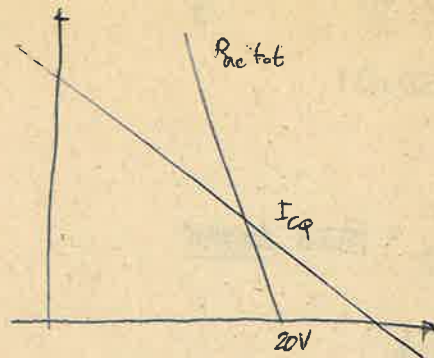$P_{\text{T}} = P_{\text{TQ}} - P_{\text{act}} = 681 - 192.5 = 489 \text{ mW}$



$R_{\text{act}} = n^2 R_{\text{L}} + R_{\text{p}} = 148 \Omega$

for max. output

$V_{\text{CQ}} = R_{\text{act}} I_{\text{CQ}}$
 $V_{\text{CQ}} = V_{\text{CC}} - I_{\text{CQ}} R_{\text{D}}$ } $I_{\text{CQ}} = \frac{V_{\text{CC}}}{R_{\text{act}} + R_{\text{D}}}$

equation 12.14

b) $I_{\text{CQ}} = \frac{20}{20 + 148} = 119 \text{ mA}$

a) $P_{\text{ac}} = \eta_{\text{t}} \frac{I_{\text{CQ}}^2 n^2 R_{\text{L}}}{2} = 1 \times \frac{0.119^2 \times (16 \times 8)}{2} = 0.9063 \text{ W}$

ideal transformer

c) $V_{\text{CEQ}} = V_{\text{CE}} - I_{\text{CQ}} R_{\text{DC}} = 17.62$
 $= 20 - 0.119 \times 20$

$P_{\text{TQ}} = 17.62 \times 0.119 = 2.0968 = 2.1 \text{ W}$